
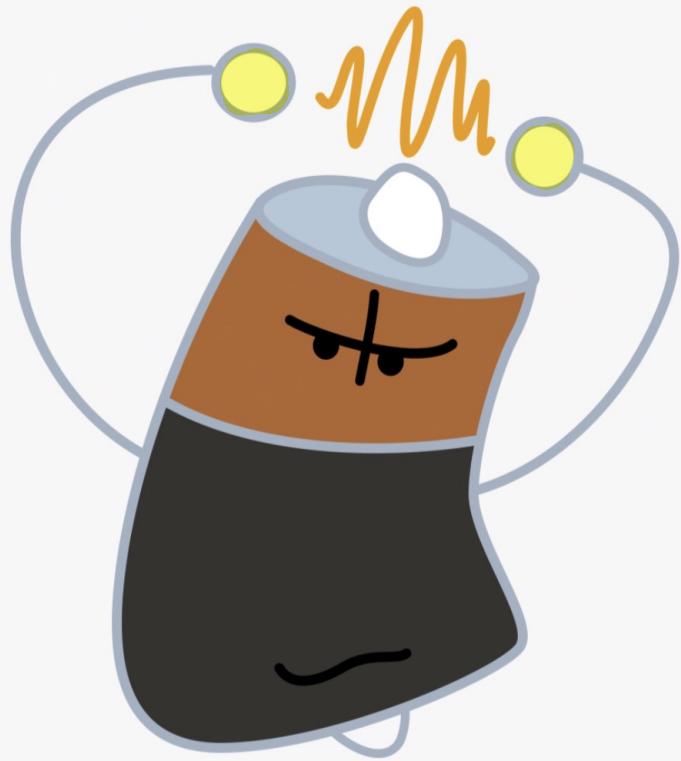


ANALOG ELECTRONIC

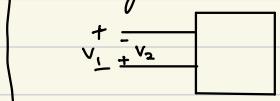


Voltage & Current


↳ Voltage (Electric force): separation of charges



$$V_2 = -V_1$$

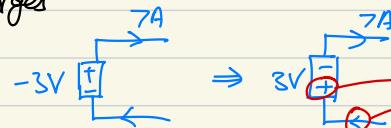


$$-3V \rightarrow 3V$$

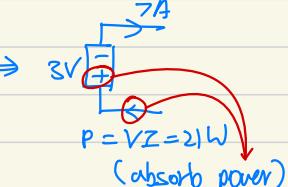

$$P = VI = 21W$$

(absorb power)

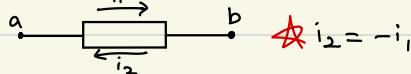↳ Current (Electric flow): motion of charges



$$i_2 = -i_1$$

✗ If current goes in from **Ove terminal**/leaves from **One terminal**





↳ source generating power \rightarrow power **Ove no.** (Active element \rightarrow batt, voltage & current sources)

✗ If current goes in from **Ove terminal**/leaves from **One terminal**

↳ source absorbing power \rightarrow power **Ove no.** (Passive element \rightarrow resistor, capacitor & inductor)

Ideal Independent sources

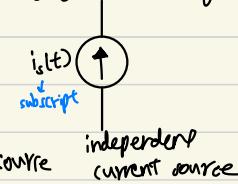
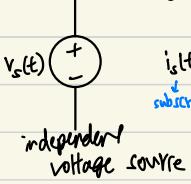
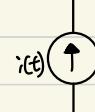
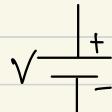
↳ establishes a voltage/current in circuit without relying on voltage/current somewhere else in circuit.



→ lower case for time varying
upper case for constant (DC)

Ideal Dependent sources

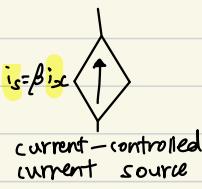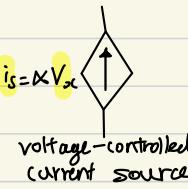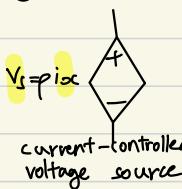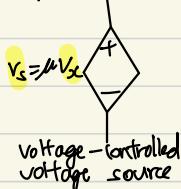↳ output is determined by voltage/current at a specific location in circuit



Series & Parallel Connections


↳ Connections that are in series share the same current

↳ Connections that are in parallel share the same voltage

✗ resistor can also be neither series/parallel

Ohm's law

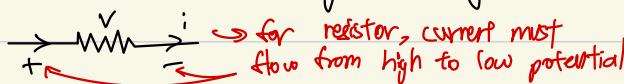$v = iR$ → refers only to **voltage & current across resistor**



→ for resistor, current must flow from high to low potential

↳ Conductance ($G = \frac{1}{R}$)

$$i = \frac{v}{R} = Gv$$

Unit is Siemens (S^{-1}/V)



Power

$$1. P = Vi$$


$$2. P = i^2 R$$

$$3. P = \frac{V^2}{R}$$

Kirchhoff's Current Law (KCL)

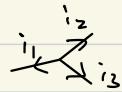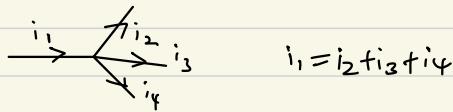

Kirchhoff's Voltage Law (KVL)

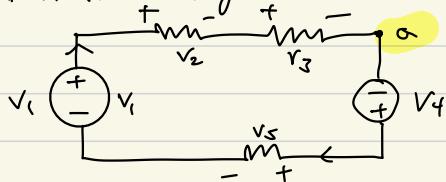


Starting from a: $+V_4 - V_3 + V_1 - V_2 - V_a = 0$

Resistor

↳ in series $\rightarrow R_{\text{eff}} = R_1 + R_2$


↳ parallel $\rightarrow R_{\text{eff}} = \frac{R_1 R_2}{R_1 + R_2}$

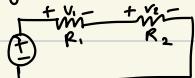→ Voltage Division for resistors in series



$$V_1 = \frac{R_1}{R_1 + R_2} V \quad \& \quad V_2 = \frac{R_2}{R_1 + R_2} V$$

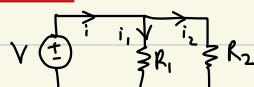→ Current Division for resistors in parallel




$$i_1 = \frac{R_2}{R_1 + R_2} i \quad \& \quad i_2 = \frac{R_1}{R_1 + R_2} i$$

Mesh Analysis


↳ Assume mesh current that flows around a mesh in a chosen direction

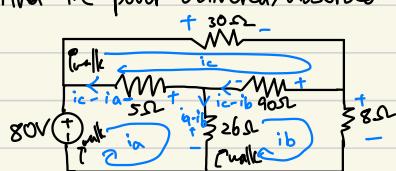E.g. Find the power delivered/absorbed by the 80V source & power dissipated by resistors.



* If have a dependent voltage source → include it in KVL.

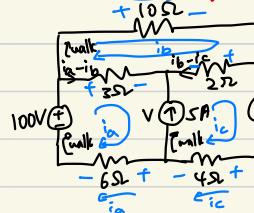* If have independent current sources, need assume it has a voltage & add in the voltage to KVL



At Need 4 independent equations
(8 unknowns)

At KVL → Mesh ia $80 + 5(i_c - i_a) - 26(i_a - i_b) = 0$

$$80 + 5i_c - 5i_a - 26i_a + 26i_b = 0$$

Mesh ib $26(i_a - i_b) + 90(i_c - i_b) - 8i_b = 0$

$$26i_a - 26i_b + 90i_c - 90i_b - 8i_b = 0$$

Mesh ic $-30 - 90(i_c - i_b) - 5(i_c - i_a) = 0$

$$-30 - 90i_c + 90i_b - 5i_c + 5i_a = 0$$

$$+100 - 3(i_a - i_b) - V - 6i_a = 0$$

$$-10i_b - 2(i_b - i_c) + 3(i_a - i_b) = 0$$


$$+V + 2(i_b - i_c) - 50 - 4i_c = 0$$

$$\star i_c = i_a + 5 \Rightarrow 5 = i_c - i_a \text{ (sum like)}$$


Norton & Thvenin's Theorem

~~★~~ Source Transformation: $V_s = i_s R$ ~~★~~

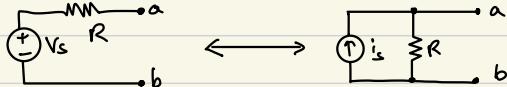voltage source in series with resistor = current source in parallel with resistor




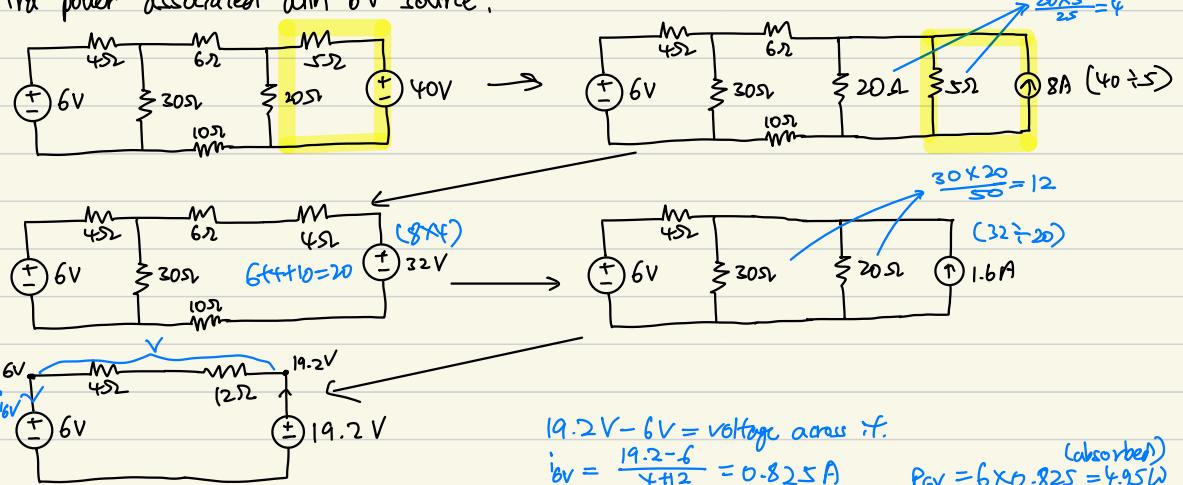E.g. Find power associated with 6V source.




Thvenin's Theorem

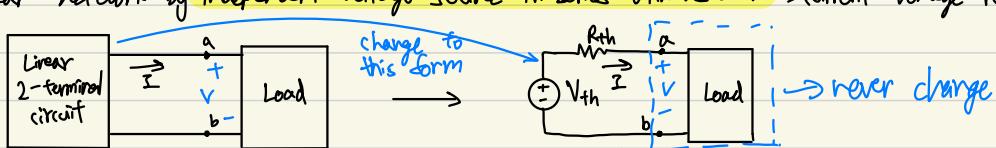↳ Replace any linear network by independent voltage source in series with resistor \rightarrow current-voltage relationship unchanged.



Norton's Theorem

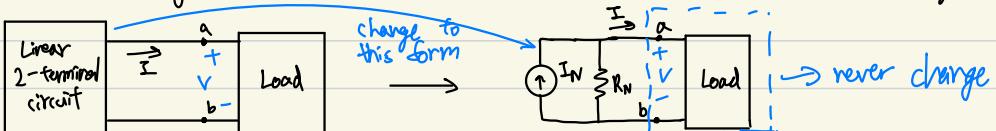↳ Replace any linear network by independent current source in parallel with resistor \rightarrow current-voltage relationship unchanged.



$$\text{R}_N = \text{R}_{th} \quad \text{I}_N = \frac{\text{V}_{th}}{\text{R}_{th}}$$



~~★~~ Method A for Determining Equivalent Circuit (No dependent sources)

To solve for $\text{R}_{th} \rightarrow$ ignore independent sources


↳ turning off independent voltage source, $\text{V}_s = 0 \rightarrow$ replace with wire \rightarrow short circuit

↳ turning off independent current source, $\text{I}_s = 0 \rightarrow$ replace with open-circuit

E.g. Find I_o using Norton's theorem

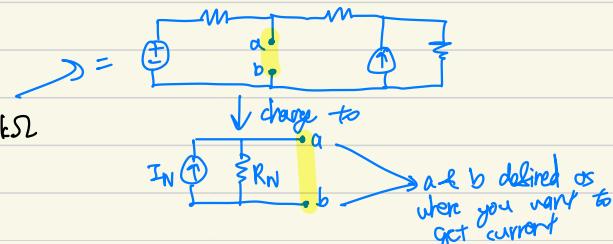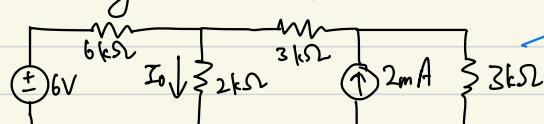

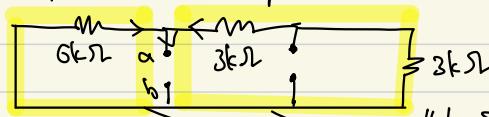1. Find $R_{th} \rightarrow$ kill all independent sources




$$R_{th} = \frac{(3+3) \times 6}{(3+3)+6} = 3k\Omega$$



parallel \rightarrow use current analysis to confirm

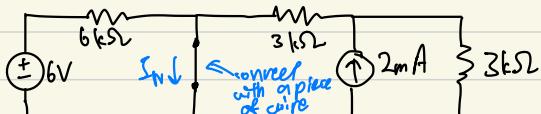2. Use mesh analysis to find I_{th} /other methods




$$I_{th} = \frac{6}{6} + \frac{3}{2+3} \times 2 = 2 \text{ mA}$$

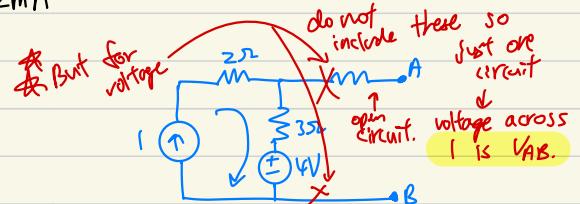3. Connect back to $2k\Omega$.

$$2 \text{ mA} \uparrow \quad 3k\Omega \quad I_{th} \downarrow \quad 2k\Omega$$

$$I_{th} = \frac{3}{3+2} \times 2 = 1.2 \text{ mA}$$



* Steps same for Thévenin Theorem, but just find $V_{th} \rightarrow$ which is across a, b \rightarrow can use mesh analysis also


Method B for Determining Equivalent Circuit (have dependent source)

↳ Terminal open-circuit voltage V_{oc} & short-circuit current I_{sc} .


↳ $R_{th} = \frac{V_{oc}}{I_{sc}}$ (Use Thévenin Theorem)

↳ similar to method A.

E.g. Find V_o for circuit shown below.

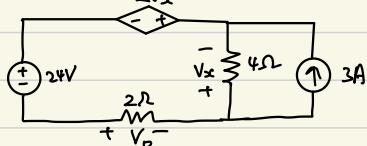


1. Find V_{oc} (V_{th})

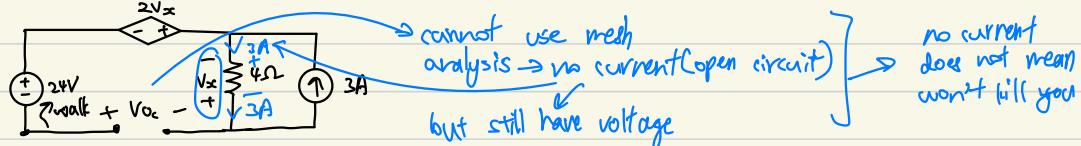

$$V_x = -3 \times 4 = -12 \text{ V}$$

$$\text{KVL: } 24 - 24 - 12 + V_{oc} = 0 \rightarrow V_{oc} = 12 \text{ V}$$

2. Find I_{sc} (I_{th})

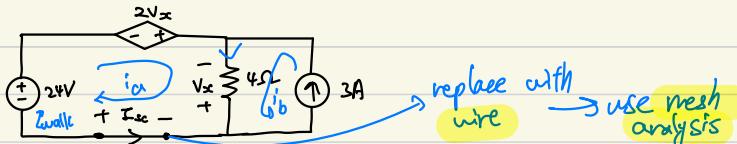

$$24 + 2V_x + V_x = 0 \rightarrow 3V_x = -24 \rightarrow V_x = -8 \text{ V}$$

$$V_x = 4 \times (-i_b + i_a)$$


$$2 = 3 + i_a \rightarrow i_a = -1 \text{ A}$$

$$I_{sc} = 1 \text{ A}$$

3. Find R_{th} & combine Thévenin equivalent circuit to load & solve V_o .

$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{12}{1} = 12 \Omega$$


$$V_{th} = V_{oc} = 12 \text{ V}$$

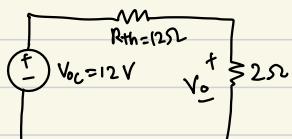

$$V_o = \frac{2}{2+12} \times 12 = \frac{12}{7} \text{ V}$$

Maximum Power Transfer

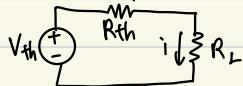Given a DC circuit \rightarrow maximum power transfer takes place when the load resistance $R_L = R_{\text{th}}$.



Proof:

P_L is max when:

$$P_L = i^2 R_L = \left(\frac{V_{\text{th}}}{R_{\text{th}} + R_L} \right)^2 \times R_L$$

$$\frac{dP_L}{dR_L} = V_{\text{th}}^2 \left(\frac{(R_{\text{th}} + R_L)^2 - R_L \times 2(R_{\text{th}} + R_L)}{(R_{\text{th}} + R_L)^4} \right) = 0$$

$$(R_{\text{th}} + R_L)^2 = 2R_L(R_{\text{th}} + R_L)$$


$$R_L = R_{\text{th}}$$

maximum power: ~~✓~~

$$P_{L,\text{max}} = \left(\frac{V_{\text{th}}}{2R_L} \right)^2$$

$$R_L = \frac{V_{\text{th}}^2}{4R_L}$$

Inductors (current flowing through)

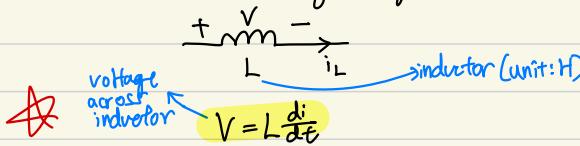

1) DC condition

$i_L = \text{constant (current)}$

$$\frac{di}{dt} = 0 \rightarrow V = 0 \quad \text{act as a piece of wire}$$

- Power & Energy

$$\text{work done} \rightarrow W_L(t_0) = \int_{-\infty}^{t_0} P dt = 0.5 L i^2(t_0) \quad \text{as } i(-\infty) = 0$$

2) Continuity

$$V \neq \infty \rightarrow \frac{di}{dt} \neq \infty$$



$\Rightarrow i_L$ cannot change instantaneously

↳ reaction of inductor slow

$$\begin{array}{c} \xrightarrow{\quad} \\ \boxed{\quad} \\ \xleftarrow{\quad} \end{array} \quad i(0-) = i(0) = i(0+) \quad \begin{array}{l} \text{before switch triggered} \\ \text{after switch open} \end{array}$$

E.g. Given that $i_1 = 1A$ at $t < 0$. Find current i_L through the R_2 resistive load when switch is closed

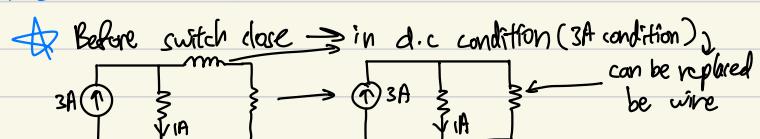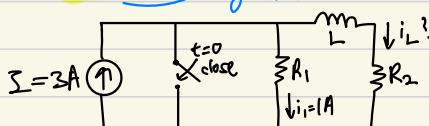at $t=0^+$. very short time after switch is closed



Before switch closed at $t=0$,

$$I = 3A \quad i_L(0-) = 3 - i_1 = 2A$$


At $t=0^+$, current shorted, $i_L(0+) = 0A$,

$$i_L(0+) = i_L(0-) = 2A \quad \text{inductor reactance immediately}$$

- Inductor in series (same $\frac{di}{dt}$) $\rightarrow L_{\text{eq}} = L_1 + L_2 + \dots + L_n$ like resistors

- Inductor in parallel $\rightarrow \frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$

Capacitors (voltage across)

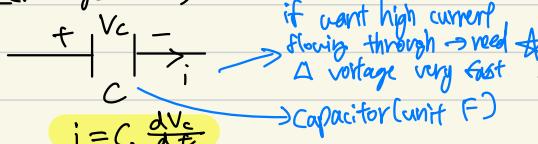

if want high current flowing through \rightarrow need ~~✓~~ Δ voltage very fast

1) DC condition

$$V_c = \text{constant} \rightarrow \frac{dV_c}{dt} = 0 \rightarrow i = 0 \quad \text{act as an open circuit}$$

2) Continuity

$$i \neq \infty \rightarrow \frac{dV_c}{dt} \neq \infty$$

$\Rightarrow V_c$ cannot change instantaneously


$$\begin{array}{c} \xrightarrow{\quad} \\ \boxed{\quad} \\ \xleftarrow{\quad} \end{array} \quad V_c(0-) = V_c(0) = V_c(0+) \quad \text{↳ capacitor react slow to } \Delta$$

- Capacitor in series $\rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$
 - Capacitor in parallel $\rightarrow C_{eq} = C_1 + C_2 + \dots + C_n$
- opposite of resistor


Natural Response of an RL Circuit inductor

↳ Natural response \rightarrow response of system when circuit has reached its constant voltage

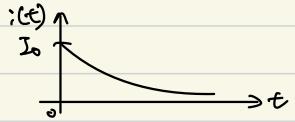& currents & is disconnected from any power source
 current through inductor $i(t) = i(0)e^{-\frac{t}{\tau}}$, $\tau = \frac{L}{R}$ that L provide
 initial current through inductor at $t=0$



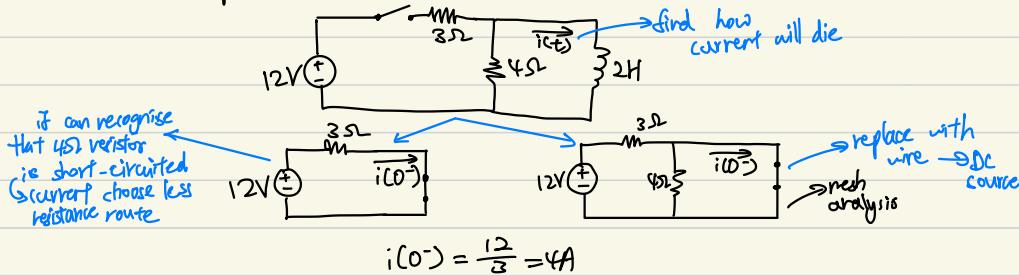E.g. The switch in the circuit shown has been closed for a long time. At $t=0$, the switch is opened. Calculate $i(t)$ for $t>0$.



Since current through inductor cannot change abruptly, $I_0 = i(0^+) = i(0^-) = 4A$.


- When $t>0 \rightarrow$ voltage source & 3Ω resistor cut off

$$i(t) = i(0^+) e^{-\frac{t}{\tau}} \quad \tau = \frac{2}{4} \\ = 4e^{-2t} A, t>0$$

E.g. The switch in the circuit has been closed for a long time before open at $t=0$. Find

- $i_L(t)$ for $t \geq 0$
- $i_o(t)$ for $t \geq 0^+$
- $v_o(t)$ for $t \geq 0^+$

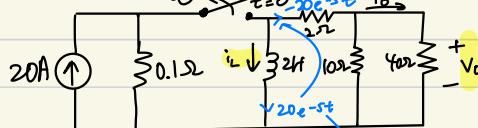d) Percentage of total energy stored in the inductor that is dissipated in the 10Ω resistor.



a) At $t=0^-$, inductor acts as short circuit causing all of the resistors to be bypassed.

$$i_L(0^-) = 20A \quad \text{At } t=0^+, i_L(0^+) = i_L(0^-) = 20A$$

$$R_{eq} = 2 + (10//40) = 10\Omega \quad \tau = \frac{L}{R_{eq}} = \frac{3}{10} = 0.3s$$

$$i_L(t) = 20e^{-5t} A, t \geq 0$$

b) Using current division,

$$i_o = -i_L \frac{10}{10+40} \quad \text{opposite of } 40\Omega$$

$$i_o(t) = -4e^{-5t} A \quad \rightarrow \frac{10}{50} \times (-20e^{-5t})$$

$$\hookrightarrow v_o = 40i_o \rightarrow v_o(t) = -160e^{-5t} V, t \geq 0^+$$

d) Initial energy stored in $2H$ inductor,

$$W_{2H}(0) = \frac{1}{2} L i^2(0) \rightarrow (20e^{-0})^2 \\ = \frac{1}{2} \times 2 \times 20^2 = 400J$$

Power dissipated by 10Ω resistor, $P_{10\Omega} = \frac{v_o^2}{10} = 2560e^{-10t} W, t \geq 0^+$

Total energy dissipated in 10Ω resistor,

$$W_{10\Omega} = \int_0^\infty 2560 e^{-10t} dt = 256 \text{ J}$$


Percentage of energy dissipated in the 10Ω resistor,

$$W_{10\Omega} = \frac{256}{400} \times 100 = 62.5\%$$

Natural Response of an RC Circuit

voltage across capacitor $V = V_0 e^{-\frac{t}{T}}$, $T = RC$, $t \geq 0$


initial voltage across capacitor

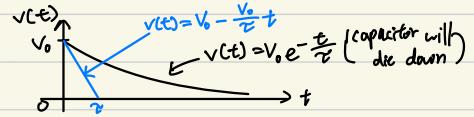


E.g. The switch in the circuit shown has been in position x for a long time. At $t=0$, the switch moves instantaneously to position y. Find

a) $v_c(t)$ for $t \geq 0$ b) $v_o(t)$ for $t \geq 0^+$ c) $i_o(t)$ for $t \geq 0^+$

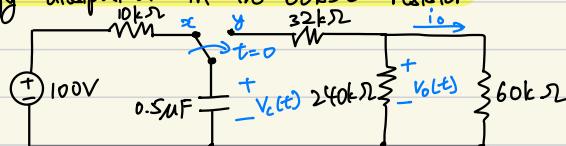d) the total energy dissipated in the $60k\Omega$ resistor



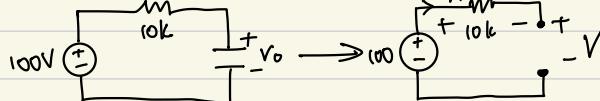a) At $t = 0^-$, switch at x \Rightarrow D.C condition \rightarrow capacitor becomes open circuit




$$R_{eq} = 32k + (240k//60k) = 80k\Omega$$

$$T = R_{eq} C = 80k \times 0.5\mu F = 40 \text{ ms}$$

$$v_c(t) = v_c(0^+) e^{-\frac{t}{T}} = 100 e^{-25t} \text{ V}, t \geq 0$$

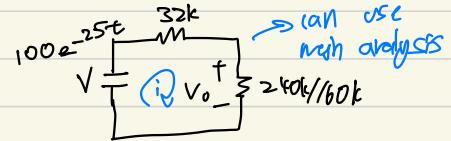b) Find $v_o(t)$ for $t \geq 0^+$, we employ voltage division method

$$V_o = \frac{240k//60k}{32k + (240k//60k)} V_c = \frac{48}{80} V_c \\ = 60e^{-25t} \text{ V}, t \geq 0^+$$



c) Take voltage across $60k\Omega$,

$$i_o = \frac{v_o}{60k} = e^{-25t} \text{ mA}, t \geq 0^+$$

d) Power dissipated in $60k\Omega$ resistor

$$P_{60k\Omega}(t) = i_o^2 \times 60k\Omega = 60e^{-50t} \text{ mW}, t \geq 0^+$$

$$\text{work done (energy)} \rightarrow W_{60k\Omega} = \int_0^\infty 60e^{-50t} dt = 1.2 \text{ mJ}$$

Step Response


when smt has changed in circuit (remove a resistor) \rightarrow see how current/voltage through conductor/capacitor react

\rightarrow when source (voltage/current) is suddenly applied to a storage device (capacitor/inductor)

\rightarrow anything that is not a natural response

remember $\xrightarrow{\text{unknown variable}} (\text{as a function of time}) = (\text{of the variable}) + [(\text{initial value}) - (\text{final value})] \times e^{-\frac{t-t_{\text{switching time}}}{T}}$

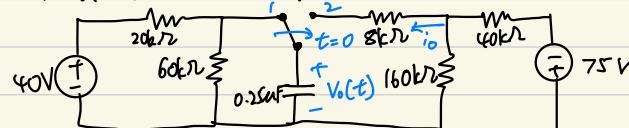E.g. The switch in the circuit has been in position 1 for a long time. At time $t=0$, it moves to position 2. Find a) $V_o(t)$ for $t \geq 0$ & b) $i_o(t)$ for $t \geq 0^+$.



a) Initial value of V_o is given by


$$V_o = \frac{60k}{20k+60k} \times 40 = 30V$$

After switch moves to position 2, at $t \rightarrow \infty$,

$$V_{\infty} = \frac{160k}{40k+160k} \times -75 = -60V$$


$$\begin{aligned} V_o(t) &= V_{\infty} + [V_o - V_{\infty}] e^{-\frac{(t-t_0)}{\tau}} \quad \tau = RC \\ &= -60 + [30 - (-60)] e^{-\frac{t}{0.01}} \\ &= -60 + 90e^{-100t} V, \quad t \geq 0 \end{aligned}$$
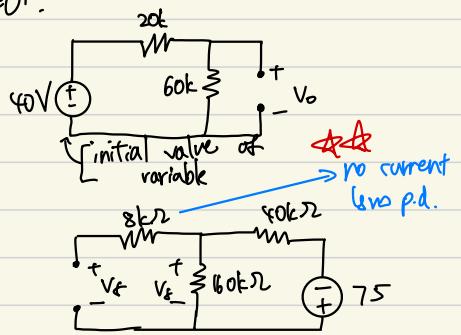
$$\begin{aligned} b) \quad i_o(t) &= C \frac{dV_o}{dt} \\ &= 0.25 \mu F \times -100 \times 90e^{-100t} \\ &= -2.25e^{-100t} \text{ mA}, \quad t \geq 0^+ \end{aligned}$$



Circuits with Two Energy Storage Elements

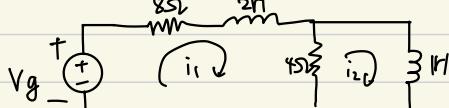Consider a circuit with two inductors \rightarrow step response



- Mesh-current equations:

$$V_g = 8i_1 + 2 \frac{di_1}{dt} + 4(i_1 - i_2) \quad \text{--- (1)}$$

$$4(i_2 - i_1) + 1 \frac{di_2}{dt} = 0 \rightarrow i_1 = 0.25 \left(\frac{di_2}{dt} + 4i_2 \right) \quad \text{--- (2)}$$

sub (2) into (1)

$$V_g = \frac{8}{4} \left(\frac{di_2}{dt} + 4i_2 \right) + \frac{1}{4} \frac{d}{dt} \left(\frac{di_2}{dt} + 4i_2 \right) + \frac{4}{4} \left(\frac{di_2}{dt} + 4i_2 \right) - 4i_2$$

$$2V_g = \frac{d^2i_2}{dt^2} + 10 \frac{di_2}{dt} + 16i_2 \rightarrow \text{use Laplace transform tool}$$


Laplace Transforms

Given time-domain function $f(t)$, its Laplace transform defined as $F(s)$.


$$\mathcal{L}\{f(t)\} = F(s) = \int_0^\infty f(t) e^{-st} dt \quad \text{formula to perform Laplace Transform on}$$

E.g. Find Laplace transform on:

a) $e^{at} u(t)$, $a \geq 0$

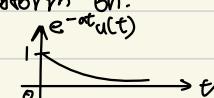

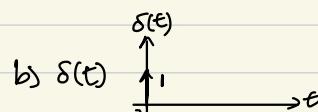
$$\begin{aligned} \mathcal{L}\{e^{at} u(t)\} &= \int_0^\infty e^{at} e^{-st} dt \\ &= \int_0^\infty e^{(a-s)t} dt \\ &= \left[-\frac{1}{a-s} e^{(a-s)t} \right]_0^\infty \\ &= -\frac{1}{a-s} (0 - (1)) = \frac{1}{s-a} \end{aligned}$$




$$\begin{aligned} \mathcal{L}\{\delta(t)\} &= \int_0^\infty \delta(t) e^{-st} dt \\ &= e^{-st}|_{t=0} \\ &= 1 \end{aligned}$$

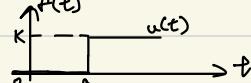E.g. Laplace transform where $f(t) = \begin{cases} 0 & \text{for } t < a \\ K & \text{for } t > a \end{cases}$



$$f(t) = K u(t-a)$$

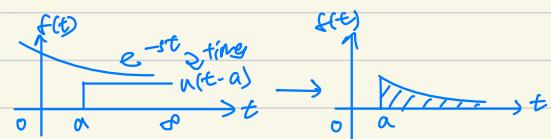

$$\begin{aligned}\mathcal{L}\{K \cdot u(t-\alpha)\} &= K \int_{\alpha}^{\infty} u(t-\alpha) e^{-st} dt \\ &= K \int_{\alpha}^{\infty} 1 \cdot e^{-st} dt \\ &= -\frac{K}{s} [e^{-st}]_{\alpha}^{\infty} \\ &= \frac{K}{s} [e^{-s\alpha} - e^{-\infty}] = \frac{Ke^{-s\alpha}}{s}\end{aligned}$$

Useful Laplace Transform Pairs

	$f(t)$	$F(s)$		
Unit impulse	δ	1		
Unit step	$u(t)$	$\frac{1}{s}$		
Unit ramp	$r(t) = t$	$\frac{1}{s^2}$		
Polynomial	$t^n, n \in \mathbb{Z}^+$	$\frac{n}{s^{n+1}}$		
Exponential	e^{-at}	$\frac{1}{s+a}$		
t-Multiplication exp.	te^{-at}	$\frac{1}{(s+a)^2}$		

	$f(t)$	$F(s)$	
Sine	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$	
Cosine	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$	
Damped Sine	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$	
Damped Cosine	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$	

Laplace Transform Properties

1. Linearity

$$\mathcal{L}\{a_1 f_1(t) + a_2 f_2(t)\} = a_1 F_1(s) + a_2 F_2(s)$$

E.g. Find Laplace transform of the function $\cos(\omega t)$ using linear property & Euler's formula

$$\cos(\omega t) = \frac{e^{j\omega t} + e^{-j\omega t}}{2} \quad [e^{j\omega t} = \cos \omega t + j \sin \omega t \quad \& \quad e^{-j\omega t} = \cos \omega t - j \sin \omega t]$$

$$\begin{aligned}\mathcal{L}\{\cos \omega t\} &= 0.5 \mathcal{L}\{e^{j\omega t} + e^{-j\omega t}\} \\ &= 0.5 \left\{ \frac{1}{s-j\omega} + \frac{1}{s+j\omega} \right\} = \frac{s}{s^2 + \omega^2}\end{aligned}$$

2. Differentiation

~~2~~ $\mathcal{L}\left\{\frac{df(t)}{dt}\right\} = sF(s) - f(0^-)$ [Laplace transform of a formula differentiated = s(Laplace transform) - initial condition]

$$\mathcal{L}\left\{\frac{d^2f(t)}{dt^2}\right\} = s \mathcal{L}\{f'(t)\} - f'(0^-) = s^2 F(s) - s f(0^-) - f''(0^-)$$

E.g. Find Laplace transform of $\sin(\omega t)$

$$\begin{aligned}\mathcal{L}\{\sin \omega t\} &= \mathcal{L}\left\{-\frac{1}{\omega} \frac{d \cos(\omega t)}{dt}\right\} = -\frac{1}{\omega} \mathcal{L}\left\{\frac{d \cos(\omega t)}{dt}\right\} \\ &= -\frac{1}{\omega} [sF(s) - f(0^-)] \\ &= -\frac{1}{\omega} [s \frac{s}{s^2 + \omega^2} - \cos(0^-)] \\ &= \frac{\omega}{s^2 + \omega^2}\end{aligned}$$

E.g. Assuming that $y(0^-)=3, y'(0^-)=2$, find $Y(s)$ from $\frac{d^2y}{dt^2} + 3 \frac{dy}{dt} + 2y = 12$

$$\begin{aligned}s^2 Y(s) - sy(0^-) - y'(0^-) + 3[sY(s) + y(0^-)] + 2Y(s) &= \frac{12}{s} \\ Y(s)[s^2 + 3s + 2] &= \frac{3s^2 + 16s + 12}{s} \\ Y(s) &= \frac{3s^2 + 16s + 12}{s(s+1)(s+2)}\end{aligned}$$

3. Integration

$$\mathcal{L}\left\{\int_0^t f(\tau) d\tau\right\} = \frac{F(s)}{s} \rightarrow \text{use Laplace response & then divide by } s$$

E.g. Use Laplace transform to find $V(s)$ if

$$v(t) + 1.6 \int_0^t v(\tau) d\tau + 0.025 \frac{dv(t)}{dt} = 5 \cos 10t, \text{ assume } v(0^-)=0$$

$$V(s) + 1.6 \frac{V(s)}{s} + 0.025 [sV(s) - v(0^-)] = \frac{5s}{s^2 + 100}$$

$$V(s)[0.025s^2 + s + 1.6] = \frac{5s^2}{s^2 + 100}$$

$$V(s) = \frac{200s^2}{(s^2 + 40s + 64)(s^2 + 100)}$$

Common Laplace Transform Properties

	$f(t)$	$F(s)$
Linearity	$c_1 f_1(t) + c_2 f_2(t)$	$c_1 F_1(s) + c_2 F_2(s)$
Differentiation	$\frac{d}{dt} f(t)$	$sF(s) - f(0^-)$
n-fold Differentiation	$\frac{d^n}{dt^n} f(t)$	$s^n F(s) - s^{n-1} f(0^-) - \dots - f^{n-1}(0^-)$
Integration	$\int_{0^-}^t f(\tau) d\tau$	$\frac{F(s)}{s}$
t-Multiplication	$tf(t)$	$-\frac{d}{ds} F(s)$
n-fold t-Multiplication	$t^n f(t)$	$(-1)^n \frac{d^n}{ds^n} F(s)$
Time shift	$f(t - t_0)u(t - t_0), t_0 > 0$	$e^{-st_0} F(s)$
Frequency shift	$e^{-s_0 t} f(t)$	$F(s + s_0)$
Time-frequency scaling	$f(ct), c > 0$	$\frac{1}{c} F\left(\frac{s}{c}\right)$
Periodic Function	$f(t) = f_1(t)u(t) + f_1(t-T)u(t-T) + \dots$	$\frac{1}{1 - e^{-sT}} F_1(s)$

Inverse Laplace Transform

↳ transform from $F(s)$ to $f(t) \rightarrow$ first decompose $F(s)$ into simple terms using Partial Fraction Expansions

1. Simple Poles

$$F(s) = \frac{N(s)}{(s+p_1)(s+p_2)\dots(s+p_n)} \rightarrow F(s) = \frac{K_1}{s+p_1} + \frac{K_2}{s+p_2} + \dots + \frac{K_n}{s+p_n} \rightarrow \text{convert back to } f(t)$$

$$K_i = [(s + p_i) \times F(s)]|_{s=p_i}$$

E.g. $F(s) = \frac{96(s+5)(s+12)}{s(s+8)(s+6)}$, find Laplace transform of $F(s)$.

$$F(s) = \frac{K_1}{s} + \frac{K_2}{s+8} + \frac{K_3}{s+6}$$

Use cover-up rule,

$$K_1 = [s \times F(s)]|_{s=0} = [\cancel{s} \times \frac{96(s+5)(s+12)}{\cancel{s}(s+8)(s+6)}]|_{s=0}$$

$$= \frac{96 \times (0+5) \times (0+12)}{(0+8) \times (0+6)} = 120$$

$$K_2 = [(s+8) \times \frac{96(s+5)(s+12)}{s(s+8)(s+6)}]|_{s=-8} = -72$$

$$K_3 = [(s+6) \times \frac{96(s+5)(s+12)}{s(s+8)(s+6)}]|_{s=-6} = 48$$

$$F(s) = \frac{120}{s} - \frac{72}{s+8} + \frac{48}{s+6} \text{ giving } f(t) = \{F(s)\} = [120 - 72e^{-8t} + 48e^{-6t}]u(t)$$

2. Order of Numerator \geq Order of Denominator

$$\text{Given } F(s) = \frac{x^2 + x + 7}{x + 8} \rightarrow F(s) = Q(s) + \frac{R(s)}{D(s)}$$

$$\text{E.g. Find } f(t) \text{ given } F(s) = \frac{5s^2 + 29s + 32}{(s+2)(s+4)}$$

$$F(s) = 5 - \frac{s+8}{(s+2)(s+4)}$$

$$= F_1(s) + F_2(s)$$

$$F_2(s) = \frac{K_1}{s+2} + \frac{K_2}{s+4} \quad \text{[Do it like above]}$$

$$\begin{aligned} & \frac{5}{s^2 + 6s + 8} = \frac{5}{(s+2)(s+4)} \\ & \frac{5}{(s+2)(s+4)} = \frac{5}{s^2 + 6s + 8} - \frac{5s^2 + 30s + 40}{s^2 + 6s + 8} \end{aligned}$$

$$f(t) = \mathcal{L}^{-1}\{F_1(s) + F_2(s)\} = f_1(t) + f_2(t)$$

$$= 5\delta(t) - 3e^{-2t}u(t) + 2e^{-4t}u(t)$$

3. Repeated Poles

$$F(s) = \frac{N(s)}{(s+p)^n} \rightarrow F(s) = \frac{K_0}{(s+p)^n} + \frac{K_{n-1}}{(s+p)^{n-1}} + \dots + \frac{K_1}{(s+p)}$$

$$K_0 = (s+p)^n F(s)|_{s=-p}$$

$$K_{n-1} = \frac{1}{1!} \frac{d}{ds} \{ (s+p)^n F(s) \}|_{s=-p} \quad \left. \right\} \text{if } n=3$$

$$K_{n-2} = \frac{1}{2!} \frac{d^2}{ds^2} \{ (s+p)^n F(s) \}|_{s=-p}$$

E.g. Find $f(t)$ given that $F(s) = \frac{100(s+25)}{s(s+5)^3}$

$$F(s) = \frac{K_1}{s} + \frac{K_2}{(s+5)} + \frac{K_3}{(s+5)^2} + \frac{K_4}{(s+5)^3} \rightarrow \text{change to partial fractions}$$

$$K_1 = s \cdot F(s)|_{s=0} = 20$$

$$K_2 = (s+5)^2 \times F(s)|_{s=-5} = -400$$

$$K_3 = \frac{1}{1!} \frac{d}{ds} \{ (s+5)^2 \times F(s) \}|_{s=-5}$$

$$= \frac{d}{ds} \left\{ \frac{100(s+25)}{s} \right\}|_{s=-5}$$

$$= 100 \left\{ \frac{s(s+25) - (s+25)(1)}{s^2} \right\}|_{s=-5} = -100$$

$$\therefore f(t) = [20 - 400 \frac{t^2}{2!} e^{-5t} - 100 \frac{t}{1!} e^{-5t} - 20e^{-5t}] u(t)$$

$$= [20 - 200t^2 e^{-5t} - 100te^{-5t} - 20e^{-5t}] u(t)$$

$$K_4 = \frac{1}{2!} \frac{d^2}{ds^2} \{ (s+5)^3 \times F(s) \}|_{s=-5}$$

$$= \frac{1}{2!} \frac{d^2}{ds^2} \left\{ \frac{100(s+25)}{s} \right\}|_{s=-5}$$

$$= 50 \frac{d}{ds} \left[\frac{-25}{s^2} \right]|_{s=-5} = -20$$

$$F(s) = \frac{20}{s} + \frac{-400}{(s+5)^2} + \frac{-100}{(s+5)^3} - \frac{20}{(s+5)^4}$$

\Rightarrow to power 3 $\rightarrow t^2$

4. Distinct Complex Poles

$$F(s) = \frac{N(s)}{(s+p_1)(s+p_2)\dots}, p_i = -(\alpha + j\beta) \text{ & } p_i^* = -(\alpha - j\beta) \rightarrow \sqrt{\alpha^2 + \beta^2}$$

$$F(s) = \frac{K}{s+p_1} + \frac{K^*}{s+p_2} \rightarrow K = (s+p_1) F(s)|_{s=-p_1} = |K| \angle 0^\circ \rightarrow \text{argument of numerator}$$

$$\mathcal{L}^{-1}\{F(s)\} = 2|K| e^{\alpha t} \cos(\beta t + \theta) u(t) \rightarrow \text{Re & real part } (\alpha \rightarrow -3)$$

E.g. Find the inverse Laplace transform of $F(s) = \frac{100(s+3)}{(s+6)(s^2+6s+25)}$

$$s = -6 \text{ & } \frac{-6 \pm \sqrt{36-100}}{2}$$

$$= -6 \text{ & } -3 \pm j4 \rightarrow \text{like } i$$

$$F(s) = \frac{K_1}{s+6} + \frac{K_2}{s-p_1} + \frac{K_2^*}{s-p_2}$$

$$K_1 = (s+6) F(s)|_{s=-6} = -12$$

$$K_2 = (s+p_1) F(s)|_{s=-p_1}$$

$$= \left[(s+3-j4) \times \frac{100(s+3)}{(s+6)(s+3-j4)(s+3+j4)} \right] \Big|_{s=-p_1 = -3+j4}$$

$$= \left[\frac{100(-p_1+3)}{(-p_1+6)(-p_1+p_2)} \right] \Big|_{-p_1 = -3+j4}$$

$$= \frac{100(j4)}{(3+j4)(j4)} = 10 \angle -53.13^\circ$$



$$\therefore f(t) = [K_1 e^{-6t} + 2|K_2| e^{\alpha t} \cos(\beta t + \theta) u(t)]$$

$$= [-12e^{-6t} + 20e^{-6t} \cos(4t - 53.13^\circ)] u(t) \rightarrow \beta \neq 0 \text{ (can't care about Re/Eve)}$$

$$p_1 = 6, p_2 = 3-j4, p_2^* = 3+j4, \alpha = -3 \text{ & } \beta = 4$$

Application of Laplace Transform for Circuit Analysis


1. Resistor (R) in s-Domain

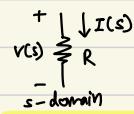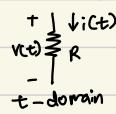

$$\text{Laplace transform: } v(t) = i(t) \times R \longrightarrow V(s) = I(s) \times R$$

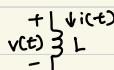2. Inductor (L) in the s-Domain

$$\text{In time domain} \longrightarrow v(t) = L \frac{di(t)}{dt}$$



Question given for final

a) final initial condition

b) convert circuit to Laplace domain

c) Find $V(s)$ or $I(s)$ mesh/KVL/KCL

d) Find $v(t)$ or $i(t)$ I12 marks

~~(*)~~ Taking Laplace transform on both sides, $V(s) = L[sI(s) - i_L(0^-)] = LsI(s) - L_i_L(0^-)$

↳ after converting to Laplace
↳ treat storage element (inductor/capacitor) like resistors

3. Capacitor (C) in the s-Domain


~~(*)~~ In time domain $\rightarrow i(t) = C \frac{dv(t)}{dt}$

Taking Laplace transform, $I(s) = C [sV(s) - v_c(0^-)]$

$$= CsV(s) - Cv_c(0^-)$$


$$V(s) = \frac{I(s) + Cv_c(0^-)}{Cs}$$
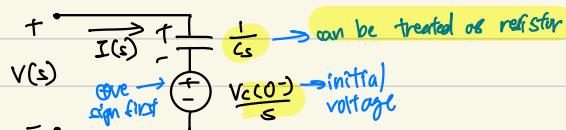
$$V(s) = \frac{1}{Cs} I(s) + \frac{v_c(0^-)}{s}$$



Circuit Solutions Without Initial Conditions

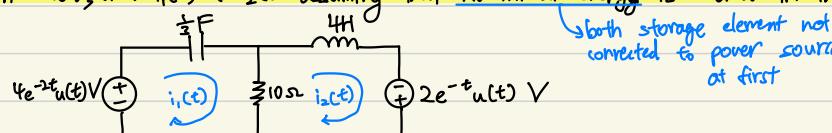
E.g. For circuit shown below, find $i_1(t)$ & $i_2(t)$ assuming that no initial energy is stored in the circuit.



Taking Laplace transform of variables,

$$4e^{-2t}u(t) \rightarrow \frac{4}{s+2}$$
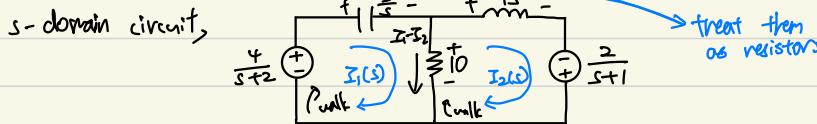
$$\frac{1}{2}F \rightarrow \frac{1}{Cs} = \frac{3}{s}$$



$$+\frac{4}{s+2} - I_1\left(\frac{3}{s}\right) - 10(I_1 - I_2) = 0 \quad (1)$$

$$+10(I_1 - I_2) - 4sI_2 + \frac{2}{s+1} = 0 \quad (2)$$

$$I_1 = \frac{2s^2(4s^2 + 19s + 20)}{20s^4 + 66s^3 + 73s^2 + 57s + 30} A$$

$$I_2 = \frac{30s^3 + 43s^2 + 6}{(s+2)(s+1)(20s^3 + 6s + 15)} A$$

use partial fraction & solve this as above


$$i_2(t) = [-0.4819e^{-2t} - 0.2414e^{-t} + 0.864e^{-0.15t} \cos(0.8529t - 33.16)] u(t) A$$

$$i_1(t) = [-0.0964e^{-2t} - 0.3448e^{-t} + 0.841e^{-0.15t} \cos(0.8529t) + 0.1977e^{-0.15t} \sin(0.8529t)] u(t) A$$

Solving Networks with Non-Zero Initial Conditions

E.g. The switch in the circuit is in the open position for a long time. At $t=0$, it is closed instantaneously.

Find $v_o(t)$ for $t>0$

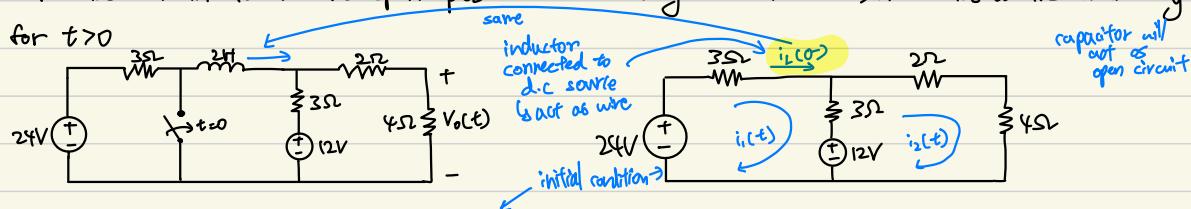

With mesh eqns, $24 = 3i_1 + 3(i_1 - i_2) + 12 \rightarrow 12 = 6i_1 - 3i_2 \quad (1)$



$$6i_2 - 12 + 3(i_2 - i_1) = 0 \rightarrow i_2 = \frac{12 + 3i_1}{9} \quad (2)$$

Sub (2) into (1), $12 = 6i_1 - 3\left[\frac{12 + 3i_1}{9}\right] \rightarrow i_1 = 3.2 A$

$$i_L(0^-) = 3.2 A$$

time-domain circuit for $t > 0$ (switch closed),

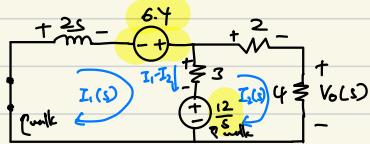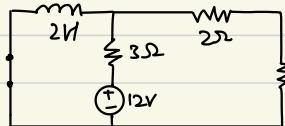If you
can add the
rest of the
circuit but
current take
least resistance path



$$2sI_1(s) - 6 \cdot 4 + 3[I_1(s) - I_2(s)] + \frac{12}{s} = 0 \quad \text{--- (1)}$$

$$2sI_2(s) + 4I_2(s) - \frac{12}{s} + 3I_2(s) - 3I_1(s) = 0 \quad \text{--- (2)}$$

$$\text{Sub (1) into (2), } I_1(s) = \frac{-\frac{12}{s} + 9I_2(s)}{2s} = -\frac{6}{s} + 3I_2(s) \quad \text{--- (3)}$$


$$\text{Sub (3) into (2), } (2s+3)[-\frac{6}{s} + 3I_2(s)] - 3I_2(s) = 6 \cdot 4 - \frac{12}{s}$$

$$I_2(s) = \frac{2 \cdot 4}{s+1}$$

$$V_0(s) = 4 \times I_2(s) = \frac{9.6}{s+1} \xrightarrow{\text{inverse Laplace transform}} V_0(t) = 9.6e^{-t} u(t), \text{ for } t > 0$$


Operational Amplifier / Op-Amp

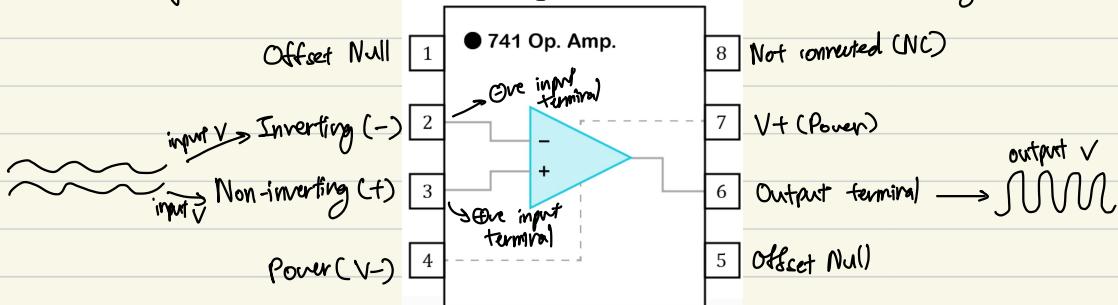- an integrated circuit that produces an output that is an amplified replica of the difference b/w 2 input voltages
- may include terminals for frequency compensation & for offset nulling.



A Typical OP-AMP Device

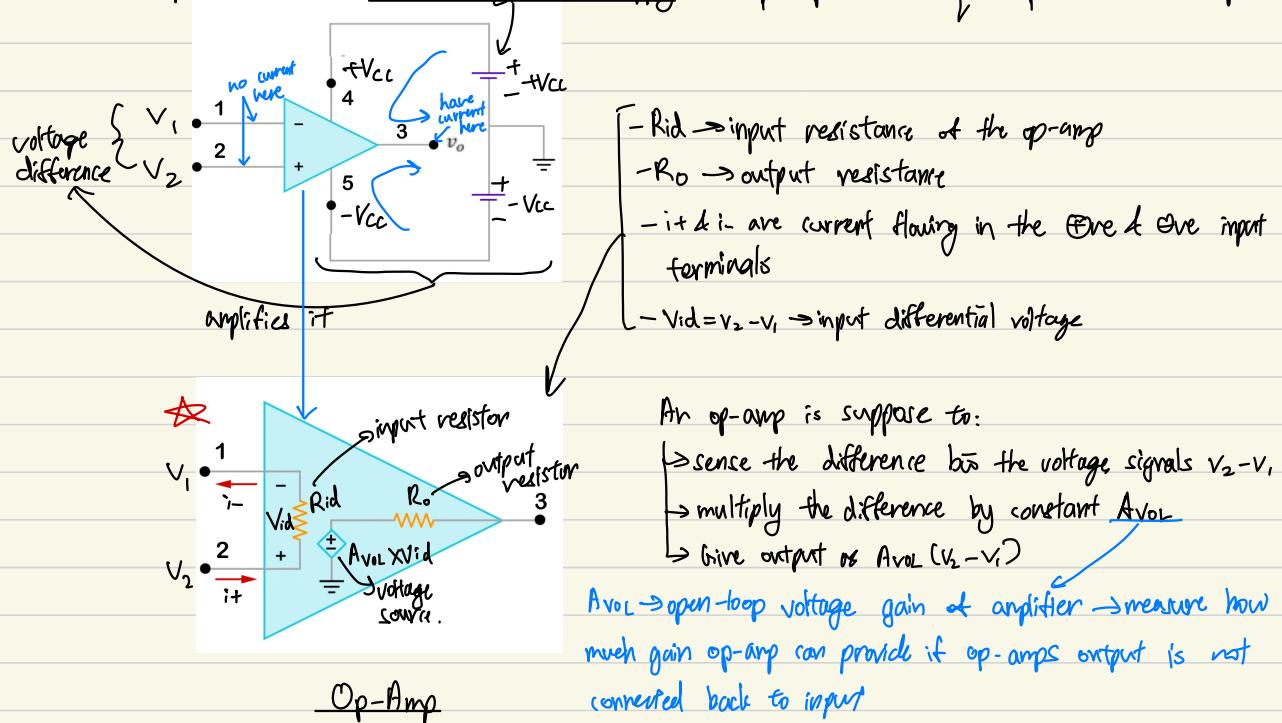→ Most IC op-amps require a dual polarity power supply (All op-amp circuit require power for their operation)



- $R_{id} \rightarrow$ input resistance of the op-amp
- $R_o \rightarrow$ output resistance
- $i+$ & $i-$ are current flowing in the ~~the~~ & ~~the~~ input terminals
- $V_{id} = V_2 - V_1 \rightarrow$ input differential voltage

An op-amp is suppose to:

- sense the difference b/w the voltage signals $V_2 - V_1$,
- multiply the difference by constant A_{vol}
- give output as $A_{vol}(V_2 - V_1)$

$A_{vol} \rightarrow$ open-loop voltage gain of amplifier → measure how much gain op-amp can provide if op-amps output is not connected back to input

Conditions of the Ideal Op-Amp

→ performance of a typical op-amp is very close to that of an ideal op-amp

1. Input resistance is infinite ($R_{id} = \infty$)

→ input connection becomes an open-circuit

2. Output resistance is zero ($R_o = 0$)

→ no voltage drop across $R_o \rightarrow$ becomes wire

3. Open-loop voltage is infinite ($A_{vol} = \infty$)


→ in order to have finite output voltage → differential input should be 0.

4. Bandwidth is infinite ($BW = \infty$)

→ no phase shift b/w input & output signals

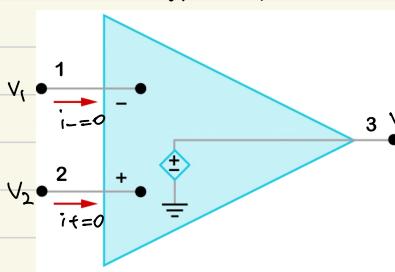5. Zero input offset voltage


$\hookrightarrow V_o = 0$ if $V_1 = V_2 / V_{id} = 0$



\leftarrow Circuit of an ideal op-amp

$$V_o = \begin{cases} +V_{cc} & \text{if } A_{vo}V_{id} > V_{cc} \\ A_{vo}(V_+ - V_-) & \text{if } -V_{cc} \leq A_{vo}V_{id} \leq V_{cc} \\ -V_{cc} & \text{if } A_{vo}V_{id} < -V_{cc} \end{cases}$$

$$V_{id} = V_+ - V_-$$

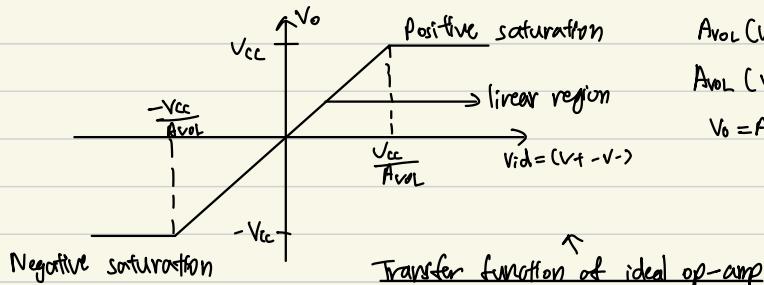

$A_{vo}(V_+ - V_-) > V_{cc} \rightarrow$ Positive saturation region


$A_{vo}(V_+ - V_-) < -V_{cc} \rightarrow$ Negative saturation region

$V_o = A_{vo}V_{id} \rightarrow$ linear region

Op-Amp Configurations

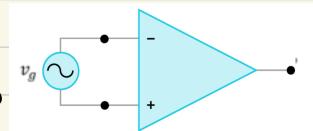* 1. Open-loop configuration (not impt) [Formula: $V_{out} = A_{vo}(V_+ - V_-)$]


\hookrightarrow output of op-amp is not fed back to the input of the op-amp



2. Closed-loop configuration

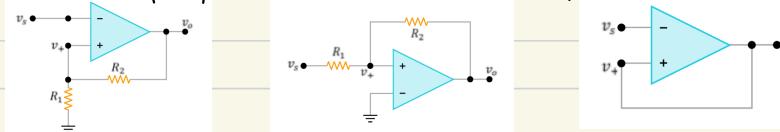
* a) Positive feedback (not impt) \rightarrow make system unstable (only want if wanna generate digital signal)

\hookrightarrow output of op-amp is fed back to the positive input terminal of op-amp



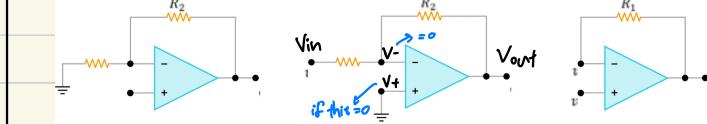* b) Negative feedback (impt)

\hookrightarrow output of op-amp is fed back to negative input terminal of op-amp




\Rightarrow ideal op-amp in negative feedback will operate in linear region: $V_o = A_{vo}(V_+ - V_-)$

$A_{vo} \rightarrow \infty$, we have $V_+ - V_- \rightarrow 0$, $V_+ = V_-$

Analyse of Inverting Feedback Amplifier Circuits

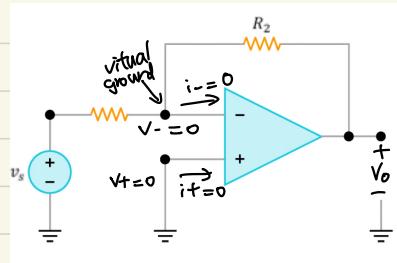E.g. You are to find V_o as a function of input voltage V_s for the amplifier circuit using an ideal op-amp




\rightarrow Negative feedback circuit \rightarrow op-amp is operating as a linear device:

$$V_+ = V_-$$

\rightarrow Ideal op-amp: $I+ = 0 \Rightarrow I- = 0$

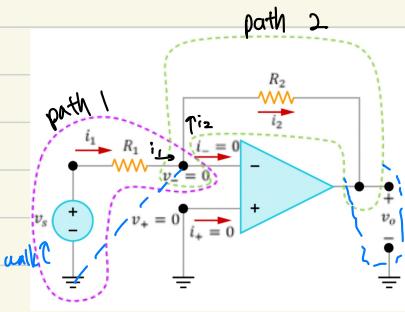\rightarrow Because V_- is not physically connected to ground \rightarrow engineers term this a virtual ground



KVL & path 1: $-V_s + i_1 R_1 = 0$

$$i_1 = \frac{V_s}{R_1}$$

KVL & path 2: $i_2 R_2 + V_o = 0$


$$i_2 = -\frac{V_o}{R_2}$$

KCL for \$v=0\$ node: $i_1 = i_2 + i_o$

$$\frac{V_s}{R_1} = -\frac{V_o}{R_2} \Rightarrow \frac{V_o}{V_s} = -\frac{R_2}{R_1}$$

(closed-loop inverting gain)

Non-Inverting Amplifier

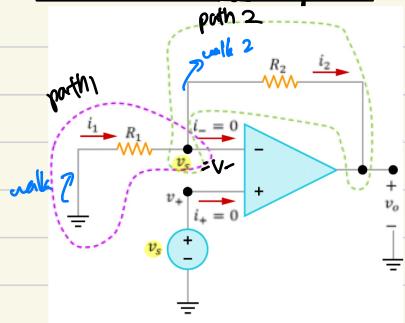

$$i_1 = i_2, v_- = V_t = V_s$$

KVL for path 1: $i_1 R_1 + V_s = 0$

$$i_1 = \frac{V_s}{R_1}$$

KVL for path 2: $-V_s + i_2 R_2 + V_o = 0$


$$i_2 = \frac{V_s - V_o}{R_2}$$

Node \$v_s\$: $i_1 = i_2 + i_o$

$$\frac{V_s}{R_1} = \frac{V_s - V_o}{R_2} \rightarrow \frac{V_s}{V_o} = 1 + \frac{R_2}{R_1}$$


Input & Output resistance

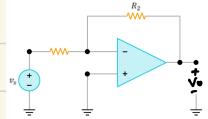Given the ideal op-amp circuit shown, what is the input & output resistance of the circuit?



Op-amp ideal $\rightarrow V_- = V_+ = 0$

a) Input resistance

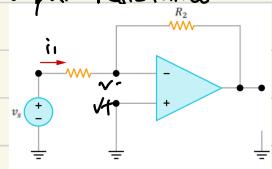


1. Define \$i_1\$.

2. Input resistance seen by \$V_s \rightarrow R_{in} = \frac{V_s}{i_1}\$

3. Take path from \$V_s\$ to \$V_-\$ we have: \$0 + V_s - i_1 R_1 = 0 \rightarrow i_1 = \frac{V_s}{R_1}\$

$$R_{in} = \frac{V_s}{i_1} = R_1 \rightarrow R_{in} = R_1$$


b) Output resistance

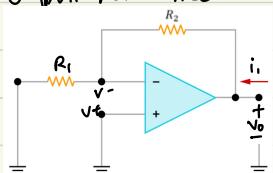

1. We know practical op-amp has resistance \$R_o\$.

2. Output resistance $\rightarrow R_{out} = \frac{V_o}{i_1} = R_o$

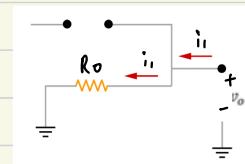3. Since ideal op-amp $\rightarrow R_{out} = 0 \Omega$



easy
Summary


Solve op-amp.

1) Define current directions

2) Use $V_+ = V_- \& I_+ = I_- = 0$

3) Figure out the KCL.

4) Equate them

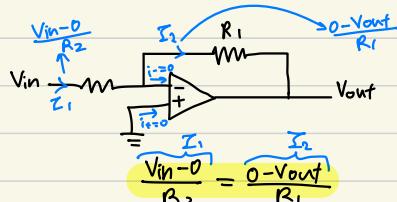


$$\frac{V_{in+} - 0}{R_2} = \frac{0 - V_{out}}{R_1}$$

If \$V_{in+}\$ is connected to \$V_{in-}\$ terminal & there is a \$+\$ sign \rightarrow correct

Op-Amp Configurations

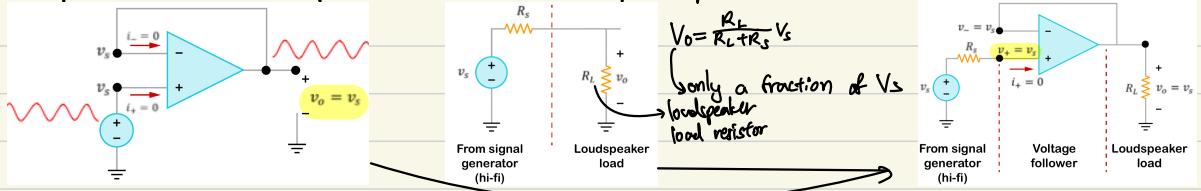
1. Voltage Follower

↳ produces an output signal that is same voltage as input, can be used to lower the output resistance of circuit
 ↳ In audio electronics → voltage follower normally used as interface b/w an amplifier circuit having high output impedance ($1k\Omega$) & loudspeaker that has a low input impedance ($4-8\Omega$)



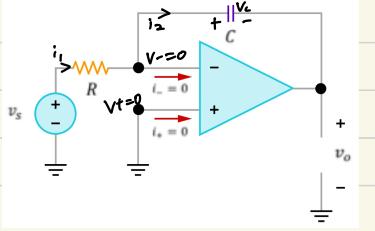2. Inverting Integrator

↳ produces an output signal that is proportionate to the integration of the input voltage w.r.t time



$$\text{current for capacitor: } i = C \frac{dv}{dt} \rightarrow \Delta V$$

$$i_1 = \frac{V_s - 0}{R} \quad i_2 = C \frac{d(0 - V_o)}{dt}$$


$$i_1 = i_2 \rightarrow \frac{V_s}{R} = C \frac{d(-V_o)}{dt}$$

$$V_s = RC \frac{d(-V_o)}{dt} \rightarrow \int_{-\infty}^t V_s(t') dt' = -RC(V_o(t))$$

$$V_o(t) = -\frac{1}{RC} \int_{-\infty}^t V_s(t') dt'$$

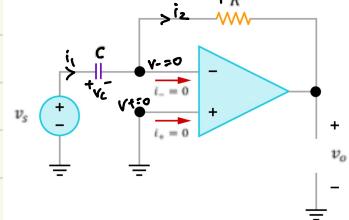3. Inverting Differentiator

↳ Produces an output signal that is proportionate to the differentiation of the input voltage over time



$$i_1 = C \frac{dv}{dt} = C \frac{d(CV_s(t) - 0)}{dt} = C \frac{d(V_s(t))}{dt}$$

$$i_2 = \frac{0 - V_o}{R} = -\frac{V_o}{R}$$

$$i_1 = i_2 \rightarrow C \frac{d(V_s(t))}{dt} = -\frac{V_o}{R}$$


$$V_o = -RC \frac{d(V_s(t))}{dt}$$

Input & Output Offset Voltage


↳ Use to address the imbalances to force the output voltage to be zero

$$V_o = A_{voh}(V_+ - V_- + V_{io}) \rightarrow \text{offset voltage}$$


Determine V_{io}

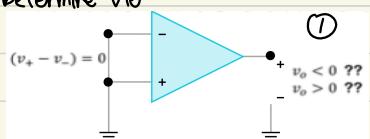

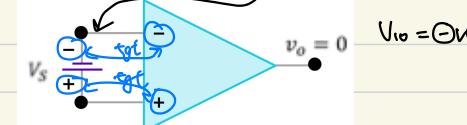$V_o < 0$ in ① → connect $V_S \rightarrow V_+ - V_- = \Theta V_C$,




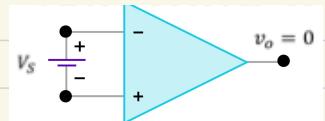$V_o > 0$ in ② → $V_o > 0, V_+ - V_- < 0$.



E.g. Consider the inverting feedback amplifier with a closed-loop gain $A_{vcl} = -5V/V$. Input signal is $V_{in} = -1V - DC$.

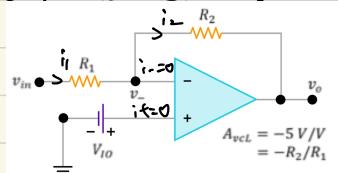Output is $5.12V - DC$. What is the V_{io} for the op-amp?



$$V_+ = V_- = V_{io}$$

$$i_1 = \frac{-1 - V_{io}}{R_1} \quad i_2 = \frac{V_{io} - 5.12}{R_2}$$

$$i_1 = i_2 \rightarrow \frac{-1 - V_{io}}{R_1} = \frac{V_{io} - 5.12}{R_2}$$


$$\frac{1 + V_{io}}{R_1} = \frac{V_{io} - 5.12}{R_2} \rightarrow \frac{R_2}{R_1} = \frac{V_{io} - 5.12}{1 + V_{io}}$$

$$-5 - 5V_{io} = V_{io} - 5.12$$

$$-6V_{io} = -0.12$$

$$V_{io} = 0.02V$$

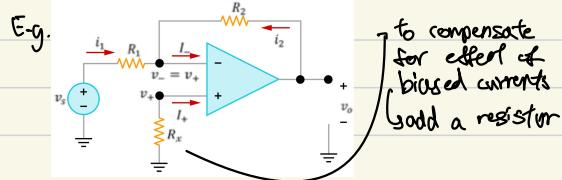- Input Bias Current $\rightarrow I_{BIAS} = \frac{1}{2}(I_+ + I_-) \rightarrow$ can be $\oplus v_e / \ominus v_e$ calculate exactly the same just $v_e = 0$, use this.
- Input Offset Current $\rightarrow I_o \neq I_- \rightarrow I_{SO} = I_+ - I_-$



Assume ideal case $\rightarrow V_+ = V_-$, except $I_+ \neq 0, I_- \neq 0$

$$V_- = V_+ = 0 - I_+ R_{f_x}$$

$$i_+ + i_2 = I_- \rightarrow \frac{V_+ - V_-}{R_1} + \frac{V_o - V_-}{R_2} = I_-$$

sub $V_- = -I_+ R_{f_x}$

$$V_o = I_- R_2 - \frac{R_2}{R_1} V_s - I_+ R_{f_x} \left(\frac{R_2}{R_1} \right)$$

$I_+ = I_- \rightarrow R_{f_x} = \frac{R_2 K_2}{R_1 + R_2} = R_1 // R_2$

$$\therefore V_o = -\frac{R_2}{R_1} V_s$$

Slew Rate (not tested)

↳ practical op-amp \rightarrow rate of A of output limited by value known as slew rate \rightarrow output of op-amp cannot Δ faster than this

$$S_R = \max \left\{ \frac{dV_o}{dt} \right\} \text{ output voltage}$$

Unit: V/ms

E.g. An op-amp with $S_R = 1 \text{ V/ms}$ is used to build an inverting amplifier with gain -10 V/V . With a 1.0 V-peak sinusoid, output has peak of 10 V .

a) At what frequency will output be affected by S_R ?

b) If sinusoidal input increased to 1.5 V at this frequency, sketch resulting waveform.

a) output voltage of sinusoidal input: $V_o = -V_s \cos \omega t$

$$\frac{dV_o}{dt} = \omega V_s \sin \omega t$$

$$\max \left\{ \frac{dV_o}{dt} \right\} = \omega V_s = 2\pi f V_s$$


$\omega V_s \leq S_R \rightarrow$ to avoid non-linear distortion

$$2\pi f V_s = S_R \rightarrow f = \frac{S_R}{2\pi V_s} = \frac{(1 \times 10^6)}{2\pi \times 10} \approx 16 \text{ kHz}$$

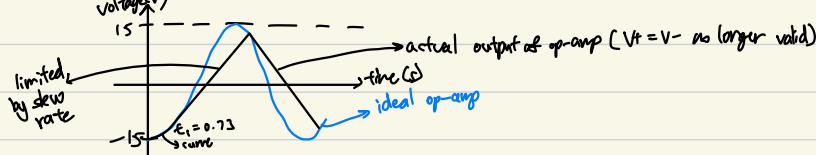b) $\omega V_s \sin \omega t \leq S_R \rightarrow \omega V_s \sin \omega t = S_R$


$$t = \frac{1}{\omega} \sin^{-1} \left(\frac{S_R}{\omega V_s} \right)$$

$$\text{voltage(V)} = \frac{1}{2\pi \times 16k} \sin^{-1} \left(\frac{1 \times 10^6}{2\pi \times 16k \times 10} \right) \approx 7.3 \text{ ms}$$



Finite Frequency Response (not tested)

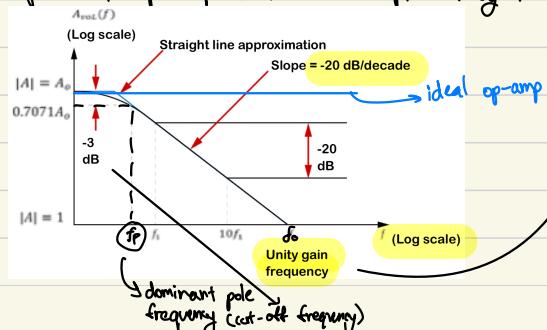↳ practical op-amp is limited \rightarrow plotted by Bode plot



$$\text{Gain of op-amp: } |A(f)| = \frac{A_0}{1 + (f/f_p)^2}$$

$$\text{When } f = f_p: |A(f)| = \frac{A_0}{\sqrt{2}} = 0.7071 A_0$$

done by setting $|A(f)| = 1 \leftarrow$ solve & find for $[f_0 \approx A_0 f_p \text{ for } A_0 \gg 1]$


gain bandwidth pte

The Ideal Diode

- Notations: DC Voltage (V_A), DC current (I_A), AC voltage (v_a), AC current (i_b)

- Sum of DC & AC components: $v_A = V_A + v_a$, $i_A = I_A + i_b$

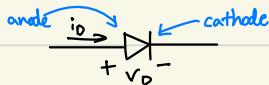↳ Diode → 2 terminal device → allow current to flow in a single direction




i_b current

1. Reverse-biased region: $V_D < 0 \rightarrow i_b = 0 \rightarrow$ act as open circuit $\rightarrow (V_D = 0, I_b = 0)$

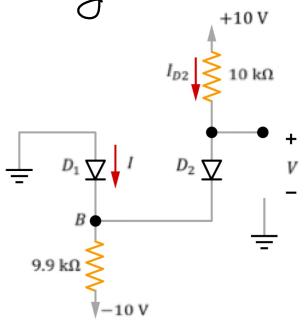2. Forward-biased region: $V_D > 0 \rightarrow i_b = \text{large} \rightarrow$ act as short circuit $\rightarrow (V_D = 0, I_b = \infty)$




E.g. Assuming diodes are ideal, find I_A & V in circuit.



1. Make assumptions

D ₁	D ₂	use this first (both are short circuit)
ON	ON	
OFF	OFF	
ON	OFF	
OFF	ON	

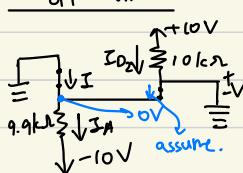

$$V = 0V$$


$$I_A = I + I_{D2}$$

$$0 - (-10) = I + \frac{10 - 0}{10k_2}$$

$$I = 0.01 \text{ mA} \rightarrow \text{So the assumption of current flow is correct}$$

* need to do again assuming D₁ is off
if negative I → assumption of current wrong

Terminal characteristic of diodes

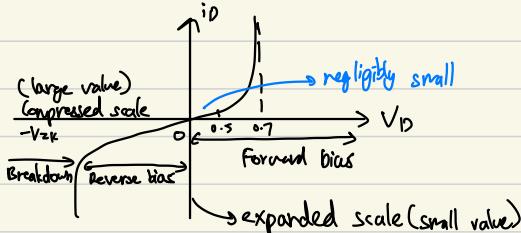

$$\rightarrow 0 < V_D < 0.5V, i_D \approx 0.$$

- Forward region → Shockley diode eqn: $i_D = I_s (e^{V_D/nV_T} - 1) \approx I_s e^{V_D/nV_T}$

→ i_D (diode current), I_s (saturation current), $n=1$ (emission coefficient), $V_T = \frac{kT}{q}$ (thermal voltage), $k=1.38 \times 10^{-23} \text{ J/K}$ (Boltzmann's constant), $q=1.602 \times 10^{-19} \text{ C}$ (electronic charge), T (absolute temperature, K)


$$V_D = nV_T \ln \frac{i_D}{I_s}$$

$$\frac{\Delta V_D}{\Delta T} \approx -2 \text{ mV/}^\circ\text{C} \rightarrow \text{for every } 1^\circ\text{C} \text{ in } T, V_D \text{ drops by } \approx 2 \text{ mV}$$

→ very small


- Reverse region → $i_D = I_s (e^{V_D/nV_T} - 1) \approx I_s$

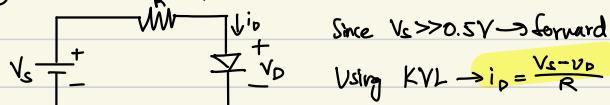E.g. Consider a simple circuit as shown, we assume that diode is operating at forward-biased region with $V_S > 0.5V$





Since $V_S > 0.5V \rightarrow$ forward-biased: $i_D = I_s e^{V_D/nV_T}$
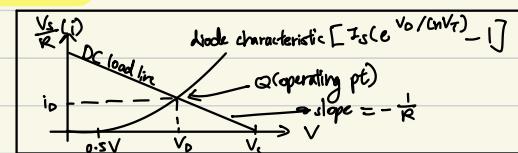
$$\text{Using KVL} \rightarrow i_D = \frac{V_S - V_D}{R}$$



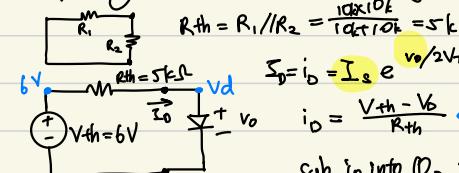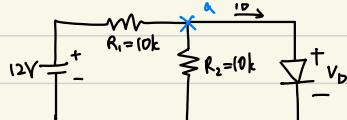E.g. Find V_D & i_D when diode is operating in forward-biased region [$I_s = 10 \text{ nA}$, $n=2$, $V_T = 26 \text{ mV}$]



$$R_{th} = R_1 // R_2 = \frac{10 \times 10k}{10k + 10k} = 5k\Omega$$

$$i_D = I_s e^{V_D/2V_T}$$

$$\ln \left(\frac{i_D}{I_s} \right) = \frac{V_D}{2V_T} \quad (1)$$

$$\text{assume } V_D = 0.7V \rightarrow \text{conducting (forward-biased)}$$

$$i_D \approx 1.06 \text{ mA}$$


$$\text{sub } i_D \text{ into } (1) \rightarrow V_D \approx 2 \times 0.026 \ln \left(\frac{1.06 \times 10^{-3}}{10 \times 10^{-9}} \right) = 0.602V$$

$$\text{until consistent}$$

$$I = 1.079 \text{ mA}, V_D = 0.603V$$

Analysis of Small-Signal Diode Circuits

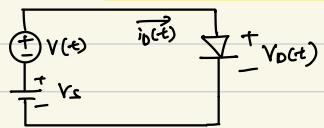↪ have a DC & AC source → but AC source generating less voltage




$$v_D(t) = V_s + v_s(t) \quad \text{sub into Shockley eqn}$$

$$i_D(t) = I_D e^{\frac{V_s(t)}{nV_T}} = I_D e^{\frac{(V_s+v_s(t))}{nV_T}} = I_D e^{\frac{V_s(t)}{nV_T}} \quad (1)$$

$$\frac{v_s(t)}{nV_T} \ll 1 \rightarrow e^{\frac{V_s(t)}{nV_T}} \approx 1 + \frac{V_s(t)}{nV_T} \quad (2)$$

small signal conductance

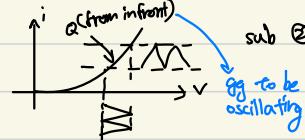


sub (2) into (1), $i_D(t) \approx I_D (1 + \frac{v_s(t)}{nV_T}) = I_D + g_d v_s(t) = I_D + i_d(t)$, $g_d = \frac{I_D}{nV_T}$

To solve this kind of question:

1. DC Analysis:

$$V_s \frac{+}{-} i_D(t) + v_{D(t)} = V_r \rightarrow \text{solve it like above}$$

2. Small-signal analysis:

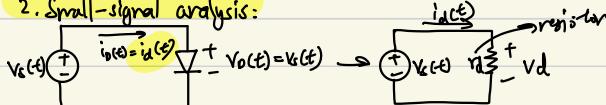

3. Superposition:


$$i_D(t) = I_D + i_d(t)$$

$$v_D(t) = V_s + v_s(t)$$

$$V_r(t) = i_d(t) r_d, \quad r_d = \frac{1}{g_d} = \frac{I_D}{nV_T}$$


Application of diode

1. Half-wave Rectifier

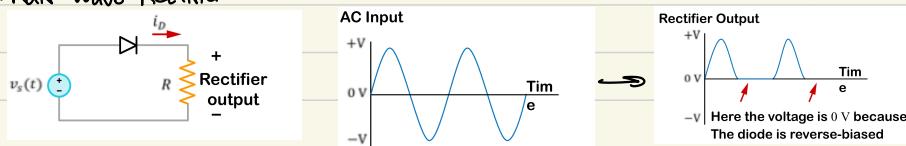


Here the voltage is 0 V because The diode is reverse-biased

2. Full-wave Rectifier

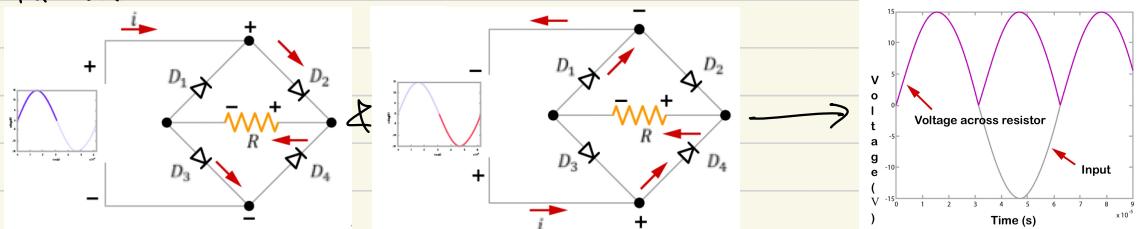

3. Elementary DC Supplies

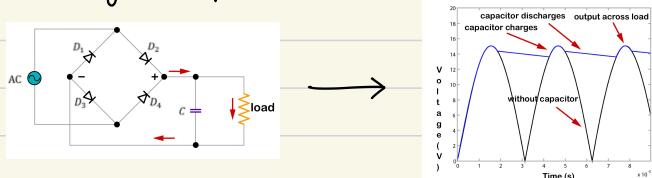


Bipolar Junction Transistor (BJTs)


↪ transistor → use of voltage b/w 2 terminals to control current flowing in 3rd terminal

↪ terminals are named: Emitter (E), Base (B) & Collector (C)

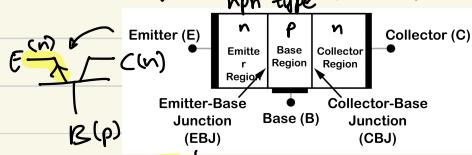↪ 2 types of BJTs: npn & pnp transistor
npn type




flow from p to n like diode

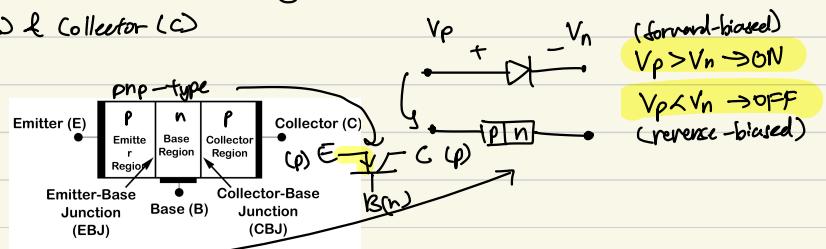

(forward-biased)
 $V_p > V_n \rightarrow \text{ON}$

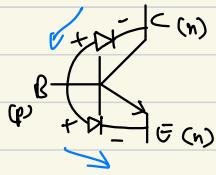$V_p < V_n \rightarrow \text{OFF}$
(reverse-biased)




BJT	status of EBJ	status of CBJ
cut-off	reverse	reverse
Active	forward	reverse
saturation	forward	forward

(Saturating conduction)

EBJ \rightarrow emitter base junction

CBJ \rightarrow collector base junction

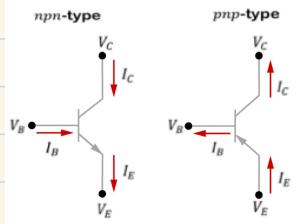Current-voltage relationship in active mode (only)



$$1) I_E = I_B + I_C$$

$$2) I_C = I_S (e^{V_{BE}/(nV_t)} - 1) \approx I_S (e^{V_{BE}/(nV_t)})$$


$$3) I_C = \beta I_B \quad \text{common emitter current gain} (\beta \geq 100, \beta \leq 200)$$

$$4) I_C = \alpha I_E \rightarrow I_C \approx I_E \quad \text{common-base current gain} (\alpha \approx 1 (0.99))$$

$$5) \alpha = \frac{\beta}{\beta+1}; \beta = \frac{\alpha}{1-\alpha}$$

When $\beta \rightarrow \infty, \alpha \rightarrow 1, I_C \rightarrow I_E$

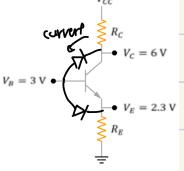E.g. Determine the mode of operation for BJT configuration shown below.



$$V_{BE} = V_B - V_E = 0.7V \rightarrow \text{ON (Forward-biased)}$$


$$V_{BC} = 3 - 6 = -3V \rightarrow \text{OFF (reverse-biased)}$$

\rightarrow BJT is in active mode

only bigger than 0.5V then ON

- Normally assume $V_{BE} \approx 0.7V$

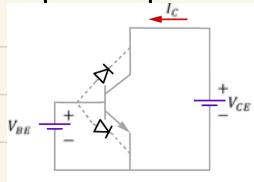Graphical Representation of BJT Characteristics




At low V_{CE} : CBJ is forward-biased \rightarrow transistor is in saturation mode

When $V_{CE} \uparrow$: CBJ becomes increasingly reverse-biased \rightarrow transistor (active)


$\hookrightarrow I_S \uparrow \rightarrow I_C \uparrow$

\hookrightarrow width of depiction region \uparrow

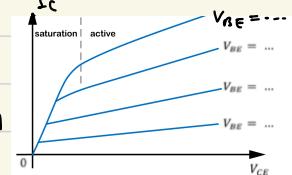$\hookrightarrow V_T$ before reaching active region



BJT Configurations

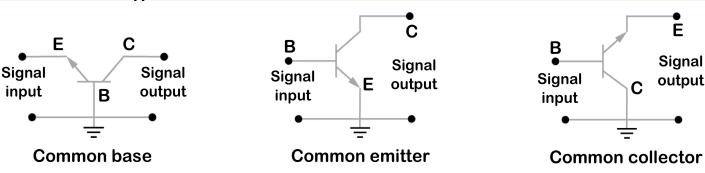

\hookrightarrow common to both input as well as output

Large Signal (DC) Analysis of BJT Circuits

E.g. The npn BJT has shown the following characteristics: $\beta = 100, V_{BE} = 0.7V$ when $I_C = 1mA$. Assuming $V_T = 2.5mV$ &

$n=1$, design the circuit so that $I_C = 2mA$ & $V_C = 5V$.

$$I_C = \frac{15 - V_C}{R_C} \rightarrow R_C = \frac{15 - 5}{2 \times 10^{-3}} = 5k\Omega$$


$$I_C = I_S e^{\frac{V_{BE}}{(nV_t)}} \rightarrow V_{BE} = nV_t \ln(\frac{I_C}{I_S})$$

$$V_{BE1} = nV_t \ln(\frac{I_{C1}}{I_S}) \rightarrow V_{BE1} = nV_t \ln(\frac{2 \times 10^{-3}}{1 \times 10^{-3}}) \rightarrow 2mA$$

$$V_{BE2} = 0.717V \quad \text{figure out } I_S \quad \text{sup in}$$

$$V_E = 0 - V_{BE2} = -0.717V$$
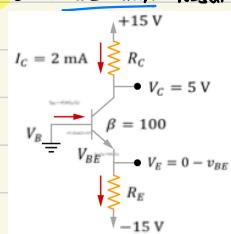
$$R_E = \frac{V_E - (-15)}{2 \times 10^{-3}} = 7.07k\Omega$$




$$\alpha = \frac{\beta}{\beta+1} = 0.99$$

$$I_E = \frac{I_C}{\alpha} = \frac{2 \times 10^{-3}}{0.99} = 2.02mA$$

→ If question say BJT in active mode, but no value of V_{BE} → assume $V_{BE} = 0.7V$

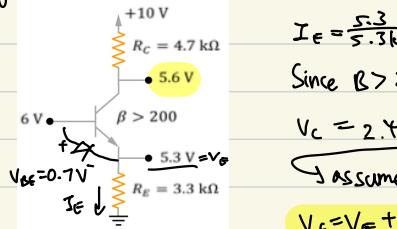E.g. Analyse given circuit & determine the voltage at all nodes & currents through all branches ($V_B, V_E, V_C = ?$; $I_B, I_E, I_C = ?$)



$$I_E = \frac{5.3}{5.3k} = 1mA$$

Since $B > 200 \rightarrow I_E \approx I_C$


$V_C = 2.48V \rightarrow$ not correct. (both diode forward-biased → saturation mode)

Assume in saturation mode, V_{CE} is normally 0.2-0.3V. Assume $V_{CE} = 0.3V$,


$$V_C = V_E + V_{CE} = 5.3 + 0.3 = 5.6V \text{ & solve the rest.}$$

transistor operating at forced $B \rightarrow \frac{I_C}{I_E} = 1.4$


~~Only can = 0 cause it = -0.7V to b~~

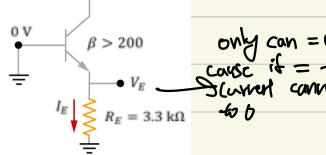

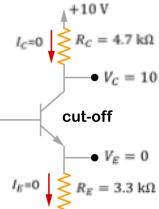only can = 0 cause it = -0.7V to b
Current cannot flow




E.g.

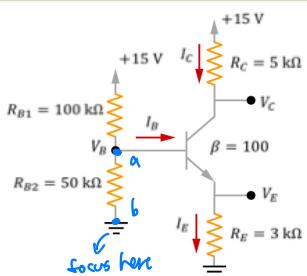

→ convert to Thevenin's equivalent
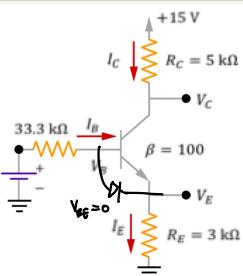
$$\begin{aligned} R_{th} &= 100k\Omega // 50k\Omega \\ V_{th} &= 150 \left(\frac{50k\Omega}{100k\Omega} \right) = 5V \end{aligned}$$



Metal-Oxide Semiconductor Field-Effect Transistor (MOSFET)


→ FET uses an electric field to control electrical behaviour

→ Both BJT & FET can be used as amplifier & switch (logical circuits)


consist of:

1. NMOS (n-channel type) → heavily-doped n region created on p-type substrate

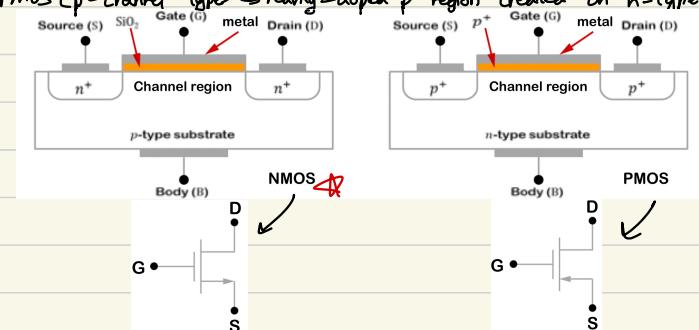2. PMOS (p-channel type) → heavily-doped p region created on n-type substrate



Inducing current flow in Channel

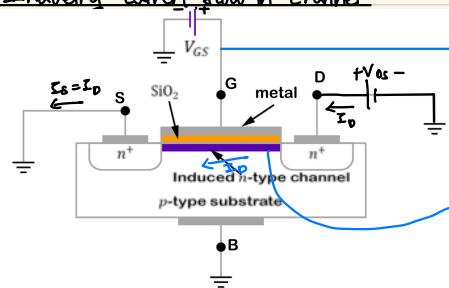

value of V_{GS} > threshold voltage (V_t)
(before no. of sufficient electrons can accumulate to form conducting channel)

magnitude of I_D dependent on V_{GS}

caused by GATE induces an electric field


controls amount of charge in channel & determine channel conductivity flowing through source & drain

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) [(V_{GS} - V_t) V_{DS} - 0.5 V_{DS}^2]$$



- w (width of induced channel), L (length of induced channel), μ_n (electron mobility $\sim 580 \text{ cm}^2/\text{V}\cdot\text{s}$), C_{ox} (oxide capacitance F/cm^2)
- $k'n = \mu_n C_{ox}$ → process transconductance parameter ($\sim 20 - 100 \text{ nA/V}^2$)
- when $V_{AS} \approx V_T$ → channel is just induced $\rightarrow I_0 \approx 0$. $V_{BS} > V_T \rightarrow$ more e^- attracted to induced channel $\rightarrow I_0 \uparrow$

Triode Region

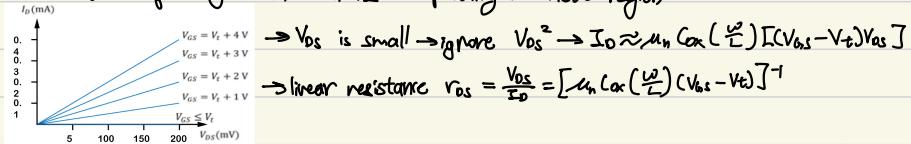↳ MOSFET operating with small V_{DS} \rightarrow operating in triode region



Saturation Person

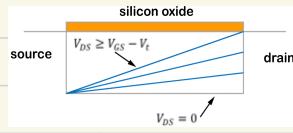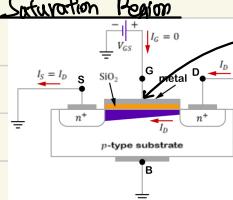


$\rightarrow V_{DS} = 0 \rightarrow$ channel said to be pinched off

$$\rightarrow V_{DS} \geq V_{GS} - V_t = V_{GS, sat} \rightarrow \text{drain current saturated}$$



$$\rightarrow I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 \rightarrow \text{sub } V_{DS} = V_{GS} - V_t$$

\rightarrow As $V_{DS} \uparrow$ above $V_{DS,off}$, $\Delta L \uparrow \&$ effective L reduces $\rightarrow I_D = \frac{1}{2} \mu n C_o \left(\frac{W}{L}\right) (V_{DS} - V_T)^2 (1 + \lambda V_{DS})$

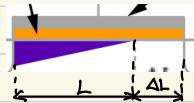($\lambda \rightarrow$ channel length modulation parameter ($0.001V^{-1} < \lambda < 0.10V^{-1}$))





Summary

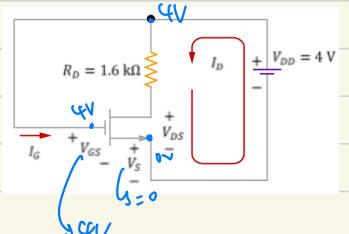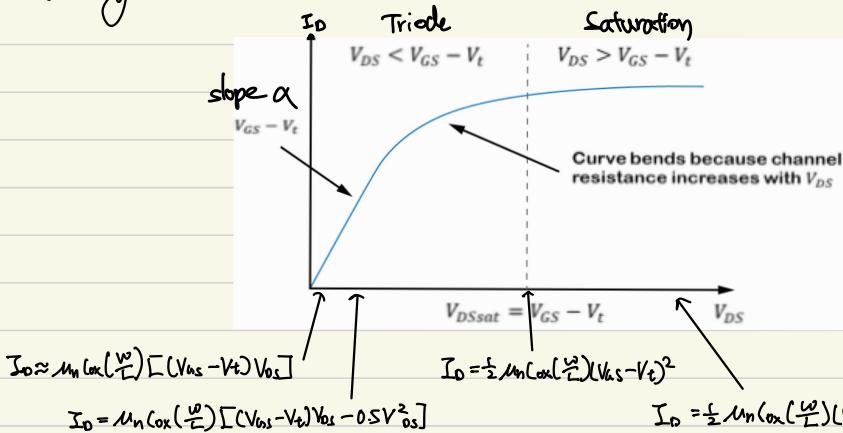

Large Signal Analysis

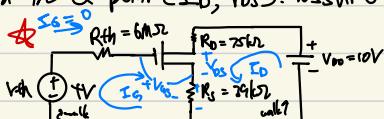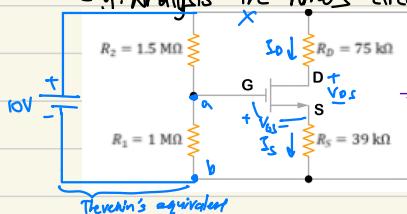E.g. Analysis the NMOS circuit & find the Q-point (I_D , V_{DS}). Assume $V_t = 1V$ & $M_n(Cox) \left(\frac{W}{L} \right) = 25 \mu A/V^2$



Assuming in saturation region find

OKV L

$$\textcircled{2} \quad I_0 = \frac{1}{2} M_n C_{\alpha x} \left(\frac{\omega}{T} \right) (V_{GS} - V_t)^2$$


$$KVL : 4 - V_{GS} - \frac{39}{I_D} (I_D) = 4$$

$$V_{AS} = -2.71, \underline{2.66}$$

$$S_0 = \frac{1}{2}(25\text{m})(2.66 - 1)^2 = 34.4\text{m}$$

10-75k (I_D)

* Is always 0.

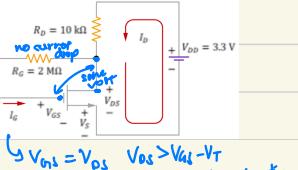

check if saturation correct: $V_{DS} \geq V_{GS} - V_T$ (satisfied) ✓


$$6.08V \quad 2.66V \quad 1V$$

If wrong ΔT_p formula &
redo calculation

AC Analysis

Inductors → open circuit $i_L = 0$
 Capacitors → short circuit $v_C = 0$

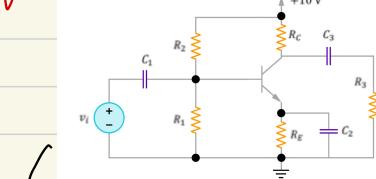BJT as Amplifier ($0.008V \rightarrow$ small signal)






→ Capacitor C_1 & C_3 are known as coupling capacitors → use to inject AC input signal & extract output signal without disturbing the Q-point


→ Capacitor C_2 bypasses capacitor → bypass R_f for AC (higher gain) → needed for good Q-point stability

DC equivalent {
 ① kill a.c. source
 ② replace capacitor with open circuit

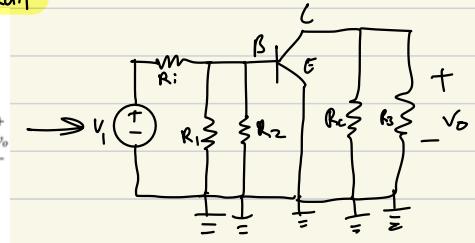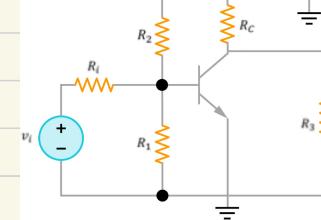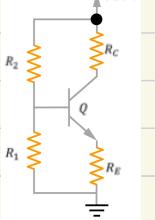AC equivalent {
 ① kill DC & connect DC to ground (+10V gone)
 ② capacitor is short circuit



Hybrid- π Model of BJT

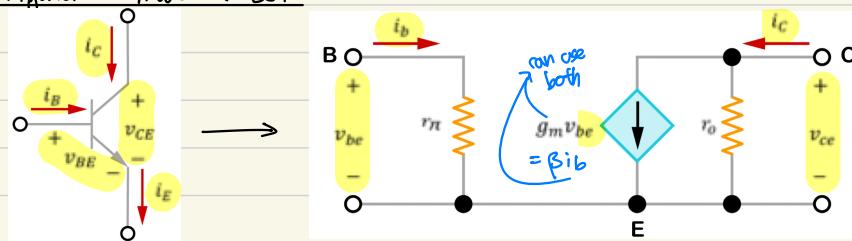

$$\Delta I_C = \beta I_B \rightarrow \text{BJT in forward-active mode}$$

$$\text{Transconductance: } g_m = \frac{I_C}{V_T}, \text{ where } V_T = \frac{kT}{q} \approx 25\text{mV}$$

$$\text{Input resistance: } r_{in} = \frac{1}{g_m} \rightarrow \text{small signal current gain} = \text{large signal current gain} (\beta = \frac{I_C}{I_B} \approx \frac{I_C}{I_B})$$


$$\text{Output resistance: } r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C} \text{ if } V_A \gg V_{CE}, V_A = \text{Early Voltage}$$

- For small signal operation to work, $|V_{BE}| \leq 5\text{mV}$




$$\Delta I_C + g_m V_{BE} = I_C + i_c$$

Small-Signal Analysis

E.g. Find the gain of the amplifier.

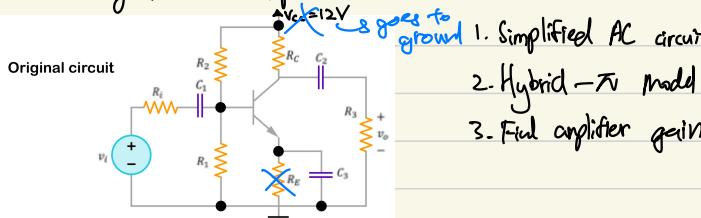

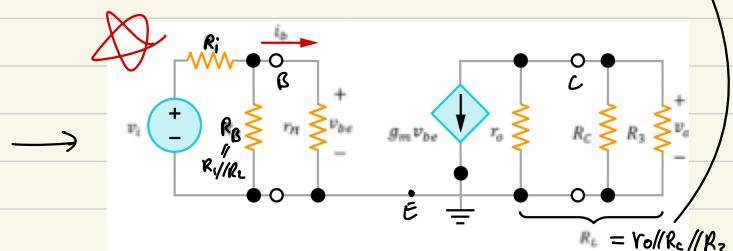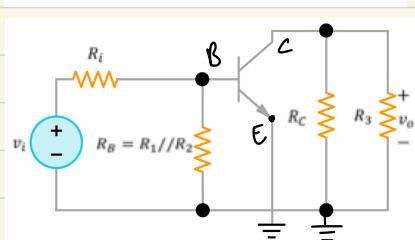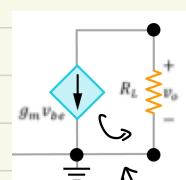1. Simplified AC circuit
2. Hybrid- π Model
3. Find amplifier gain




$$\text{Gain} = \frac{V_o}{V_i} = \frac{V_o}{V_{BE}} \frac{V_{BE}}{V_i}$$


$$V_o = -g_m V_{BE} R_L \rightarrow \frac{V_o}{V_{BE}} = -g_m R_L \quad \text{①}$$

$$V_{BE} = \frac{r_\pi // R_1 // R_2}{R_i + r_\pi // R_1 // R_2} \times V_i \rightarrow \frac{V_{BE}}{V_i} = \frac{r_\pi // R_1 // R_2}{R_i + r_\pi // R_1 // R_2} \quad \text{②}$$

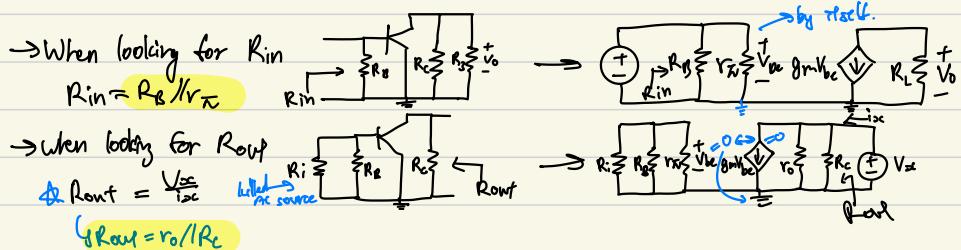
$$\text{Gain} = A_v = -g_m R_L \left(\frac{R_o // r_\pi}{R_i + (R_o // r_\pi)} \right)$$




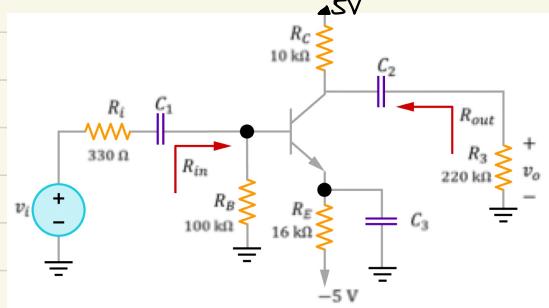
E.g. Given that common emitter current gain is $\beta=65$ & early voltage $V_A=50V$, find the voltage gain, input & output resistances of circuit. Assume that $V_{BE}=0.7V$, $V_T=25mV$ & that the BJT is biased for small-signal operation.



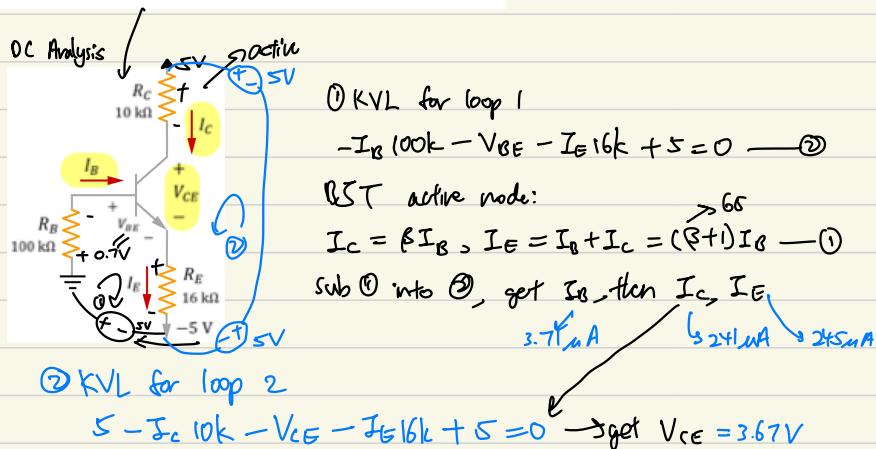① DC analysis → Q point (I_B , I_C , V_{CE})
 ② AC analysis ← r_o , r_π , g_m



AC Analysis

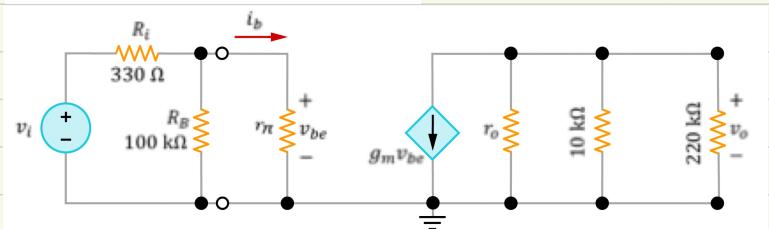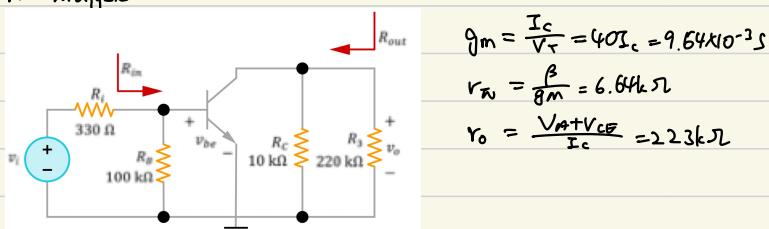

$$\text{Gain} = -g_m (r_o // 10k // 220k) \left(\frac{r_\pi // R_B}{R_i + r_\pi // R_B} \right)$$

$$= -83.8 V/V$$


$$\text{Gain} = \frac{V_o}{V_i}$$

$$V_o = -g_m V_{BE} (r_o // 10k // 220k)$$


$$\frac{V_o}{V_{CE}} = -g_m (r_o // 10k // 220k)$$

$$V_{BE} = \frac{r_\pi // R_B}{R_i + r_\pi // R_B} V_i$$

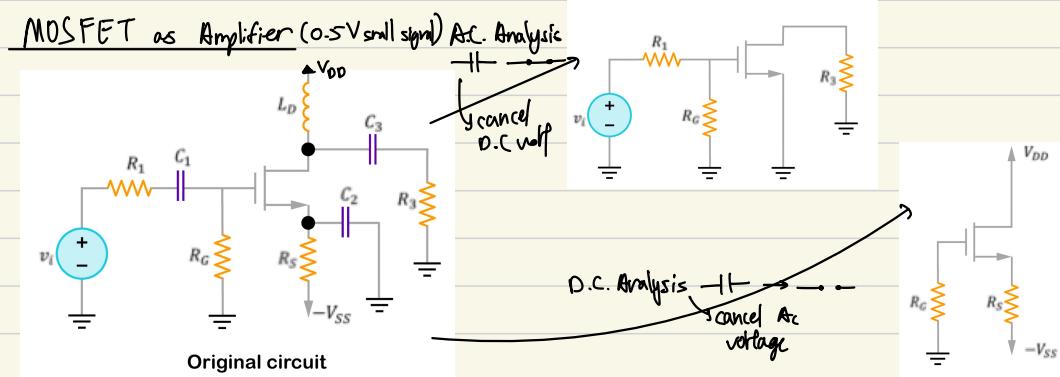
$$\frac{V_{CE}}{V_i} = \frac{r_\pi // R_B}{R_i + r_\pi // R_B}$$




Small-signal Model of MOSFET Amplifier

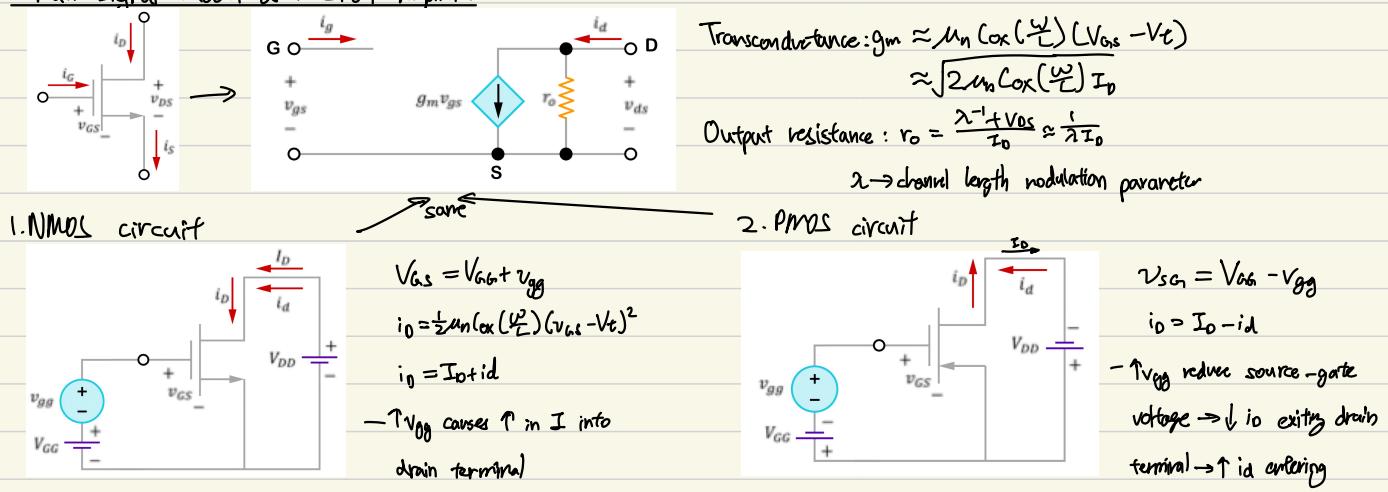

Hybrid- π model

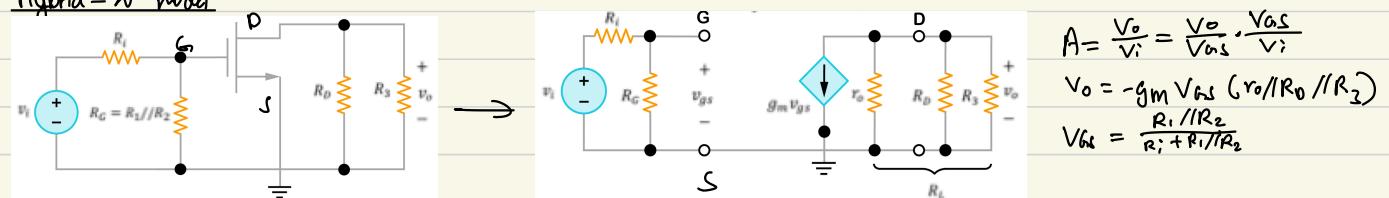


→ R_{in} & R_{out} created like above.

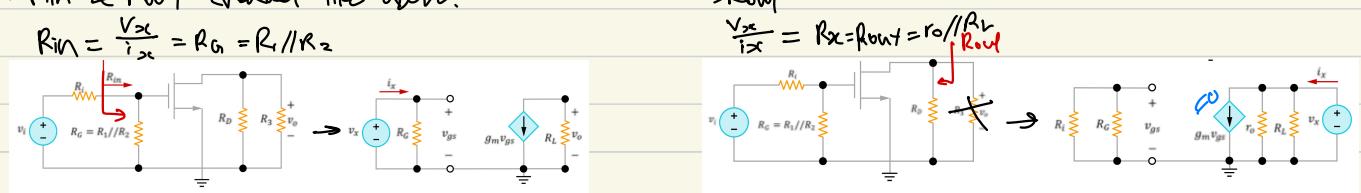

Small-signal analysis

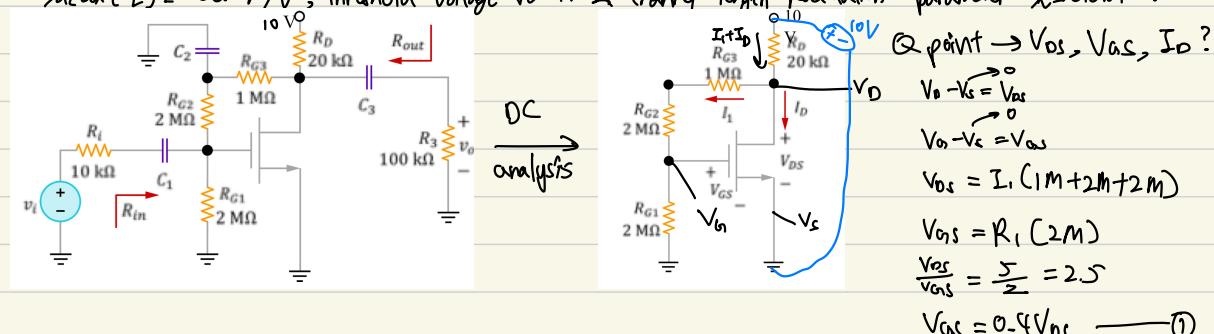E.g. Find the voltage gain, input & output resistances of the NMOS circuit as shown below. Assume that $\mu_n C_{ox} (\frac{W}{L}) = 500 \mu A/V^2$, threshold voltage $V_t = 1V$ & channel length modulation parameter $\lambda = 0.0167V^{-1}$.




$$I_D = \frac{1}{2} M_c L_0 \times \left(\frac{V_D}{L_0} \right) (V_{DS} - V_T)^2 \quad \text{--- (2)}$$

$$-10V + R_D (I_1 + I_D) + V_{DS} = 0 \quad \text{--- (3) (KVL loop)}$$

$$I_1 = \frac{V_{DS}}{5M} \quad \text{--- (4)}$$

sub (1), (2), (4) into (3) & solve to get the rest

AC analysis

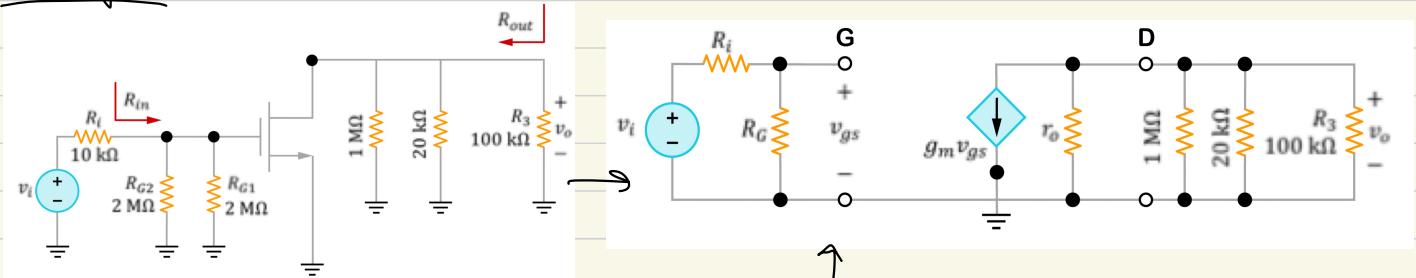

$A = \frac{v_o}{v_i}$ & get R_{in} & R_{out} by replacing them in